

ECE 550D

Fundamentals of Computer Systems and Engineering

Fall 2023

Storage and Clocking


Xin Li & Dawei Liu
Duke Kunshan University

Slides are derived from work by
Andrew Hilton, Tyler Bletsch and Rabi Younes (Duke)



Last time...

- Who can remind us what we did last time?
 - SR latch
 - D latch
 - Clocks


 
Building up to the D Flip-Flop and beyond





SR Latch
(too awkward)

  

D Latch
(bad timing)

  

D Flip-Flop
(okay but only one bit)

  


Register
(nice!)

3

DFF: Edge Triggered

- Instead of level triggered
 - Latch a new value at a clock level (high or low)
- We use edge triggered
 - Latch a value at a clock edge (rising or falling)


Falling Edges

 

Rising Edges

4


Our Ultimate Goal: D Flip-Flop

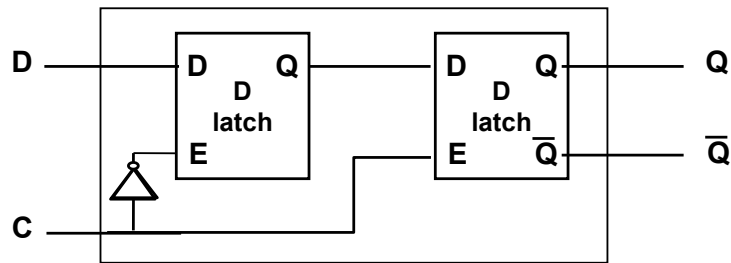

- Rising edge triggered D Flip-flop
 - Two D Latches w/ opposite clking of enables

5


D Flip-Flop

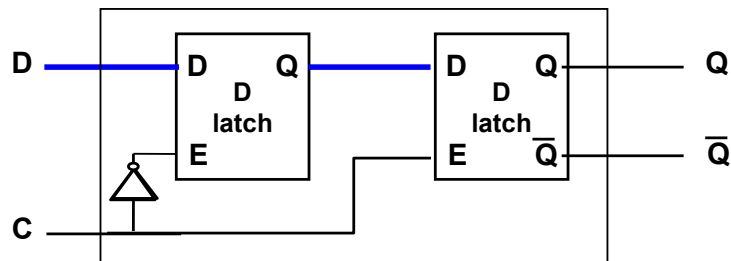

- Rising edge triggered D Flip-flop
 - Two D Latches w/ opposite clking of enables
 - On Low Clk, first latch enabled (propagates value)
 - Second not enabled, maintains value

6


D Flip-Flop

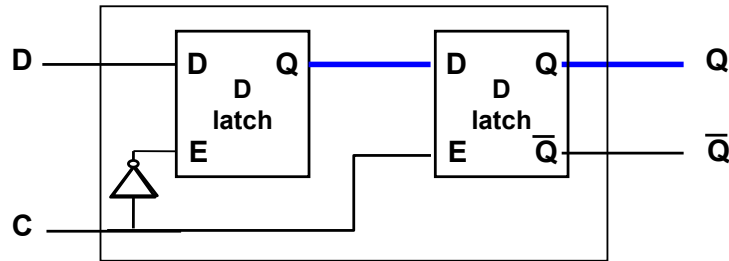

- Rising edge triggered D Flip-flop
 - Two D Latches w/ opposite clking of enables
 - On Low Clk, first latch enabled (propagates value)
 - Second not enabled, maintains value
 - On High Clk, second latch enabled
 - First latch not enabled, maintains value

7

D Flip-Flop

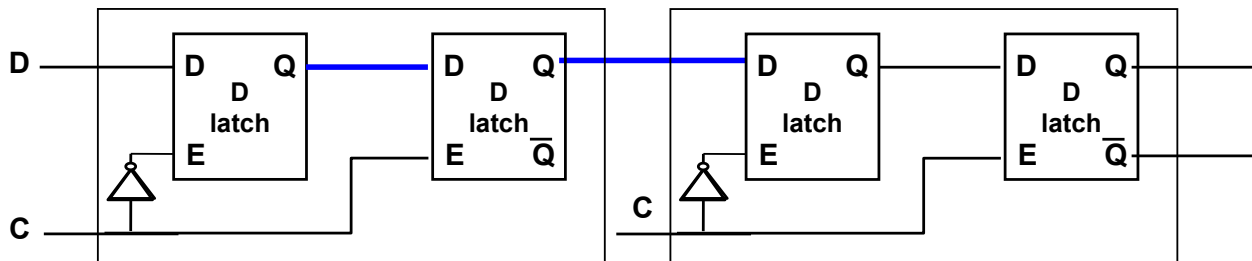

- No possibility of "races" anymore
 - Even if I put 2 DFFs back-to-back...
 - By the time signal gets through 2nd latch of 1st DFF
1st latch of 2nd DFF is disabled
- Still must ensure signals reach DFF before clk rises
 - Important concern in logic design "making timing"

8




D Flip-flops

- Could also do falling edge triggered
 - Switch which latch has NOT on clk
- D Flip-flop is ubiquitous
 - Typically people just say “latch” and mean DFF
 - Which edge: doesn't matter
 - As long as consistent in entire design
 - We'll use rising edge

9

D flip flops

   - Generally don't draw clk input
 - Have one global clk, assume it goes there
 - Often see > as symbol meaning clk
- Maybe have explicit enable
 - Might not want to write every cycle
 - If no enable signal shown, implies always enabled



- Get output and NOT(output) for “free”

10

A few words about timing

- Quartus will tell you what timing you make
 - Fmax : how fast can this be clocked
 - Tells you your worst timing paths
 - From which dff to which dff
 - Can see in schematic viewer (usually)


11

Fixing timing misses

- Typical approach: reduce logic (gate delays)
 - Better adder?
 - Rethink approach?
 - Change "don't care" behavior?
- Fix high fanout
 - Duplicate high FO/simple logic
- Also, feel free to ask for help from me/TAs
 - Quartus's tools to help you fix them aren't the best



12

 Building up to the D Flip-Flop and beyond





SR Latch

(too awkward)

  



D Latch

(bad timing)

  

D Flip-Flop


(okay but only one bit)

  



Register

(nice!)

 Stick a bunch of DFFs together to make a register




Next evolution: multiple registers

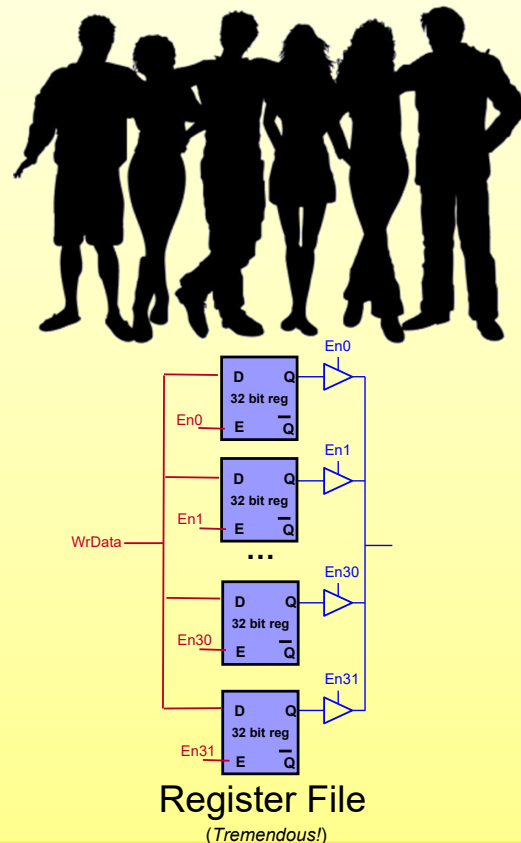 

Register File

- Can store one value... How about many?
- Register File
 - In processor, holds values it computes on
 - MIPS, 32 32-bit registers
- What other components do we need?

Register File: Interface

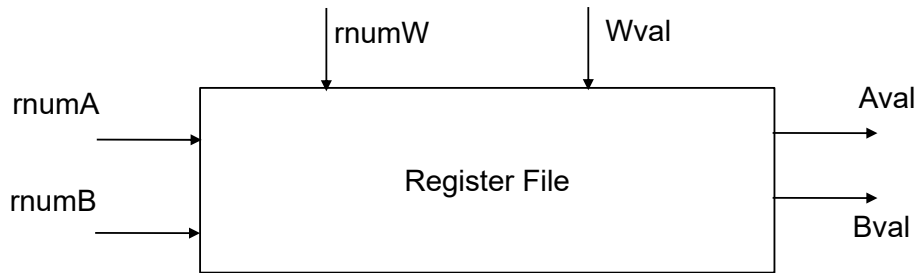


- 4 inputs
 - 3 register numbers (5 bit): 2 read, 1 write
 - 1 register write value (32 bits)
- 2 outputs
 - 2 register values (32 bits)

17

Register File Design

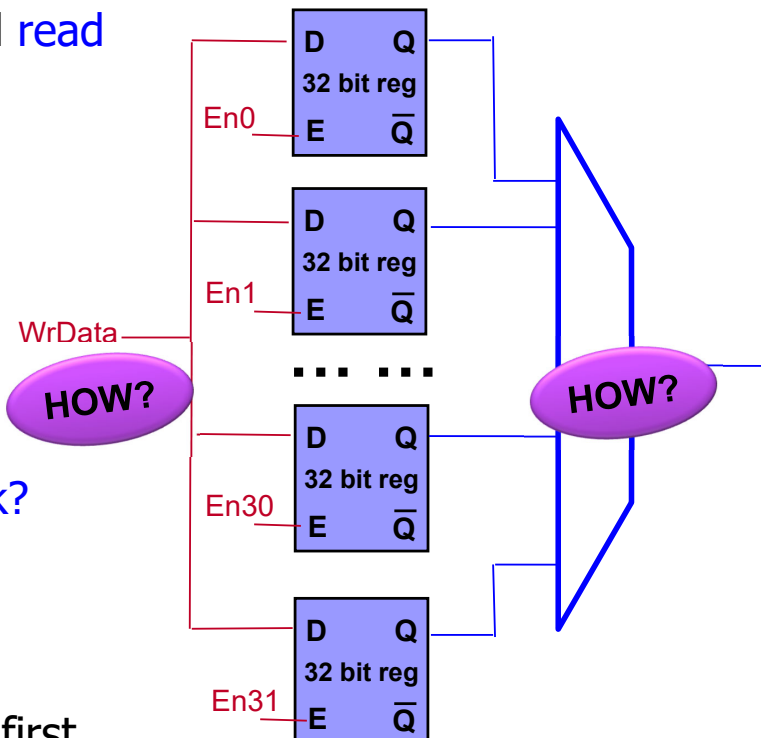
- Two problems: **write** and **read**
- **Writing** the registers
 - Need to pick which reg
 - Have reg num (e.g., 19)
 - Need to make $En_{19}=1$
 - $En_0, En_1, \dots = 0$
- **Read**: Use a mux to pick?
 - 32-input mux = slow
 - Need a better method...
- Let's talk about **writing** first.



18

First: A Decoder

 
- First task: convert binary number to “one hot”
 - Saw this before
 - Take register number



19

Register File

 
- Now we know how to **write**:
 - Use decoder to convert reg # to one hot
 - Send write data to all regs
 - Use one hot encoding of reg # to enable right reg
- Still need to fix **read** side
 - 32 input mux (the way we've made it) not realistic
 - To do this: expand our world from {1,0} to {1, 0, **Z**}



20

So this third option: Z

 
- There is a third possibility: Z ("high impedance")
 - Output is "disconnected"
- Gate that gives us Z : **Tri-state**



D	E	Q
0	1	0
1	1	1
-	0	Z

21

CMOS: Complementary MOS

 


- 2 inputs: E and D. What does this do?
 - Write truth table for output

E	D	Output
0	0	
0	1	
1	0	
1	1	

22

CMOS: Complementary MOS

 


- 2 inputs: E and D. What does this do?
 - Write truth table for output
 - When E = 1, straightforward

E	D	Output
0	0	
0	1	
1	0	1
1	1	0

23

CMOS: Complementary MOS

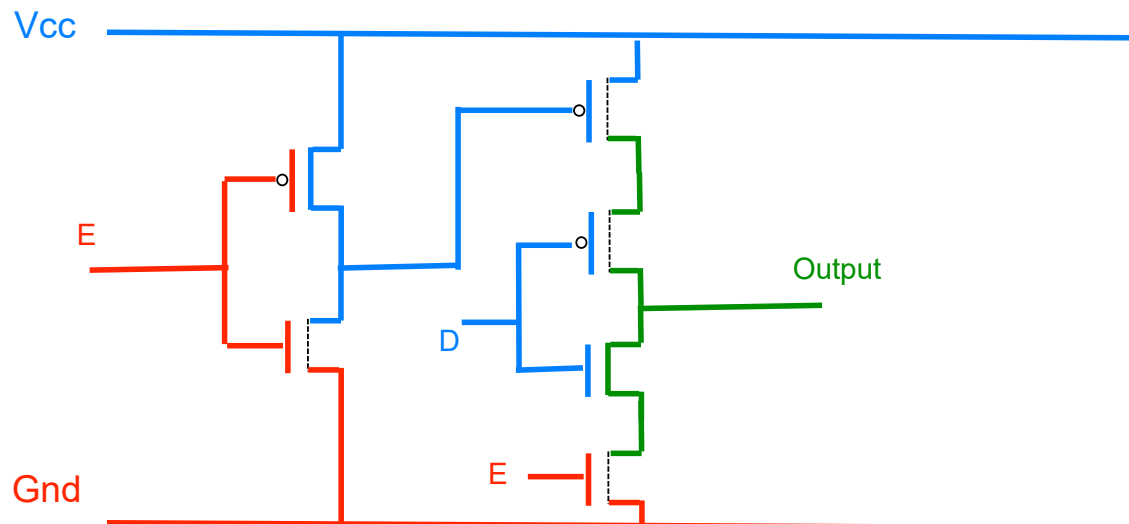


- 2 inputs: E and D. What does this do?
 - Write truth table for output
 - When E = 1, straightforward
 - When E = 0, no connection: Z

E	D	Output
0	0	Z
0	1	Z
1	0	1
1	1	0

24

High Impedance: Z

 - Z = High Impedance
 - No path to power or ground
 - "Gate" does not produce a 1 or a 0
- Previous slide: **tri-state** inverter
 - More commonly drawn: tri-state buffer
 - E = enable, D = data




D	E	Out
0	1	0
1	1	1
X	0	Z

X="Don't care"

25

Remember this rule?

 - Remember I told you not to connect two outputs?




- If one gate tries to drive a 1 and the other drives a 0
 - "Short circuit" — lots of current -> lots of heat

26

We've had this rule one day... and you break it

It's ok to connect multiple outputs together
Under one circumstance:

 
All but one must be outputting Z at any time



27

Mux, implemented with tri-states

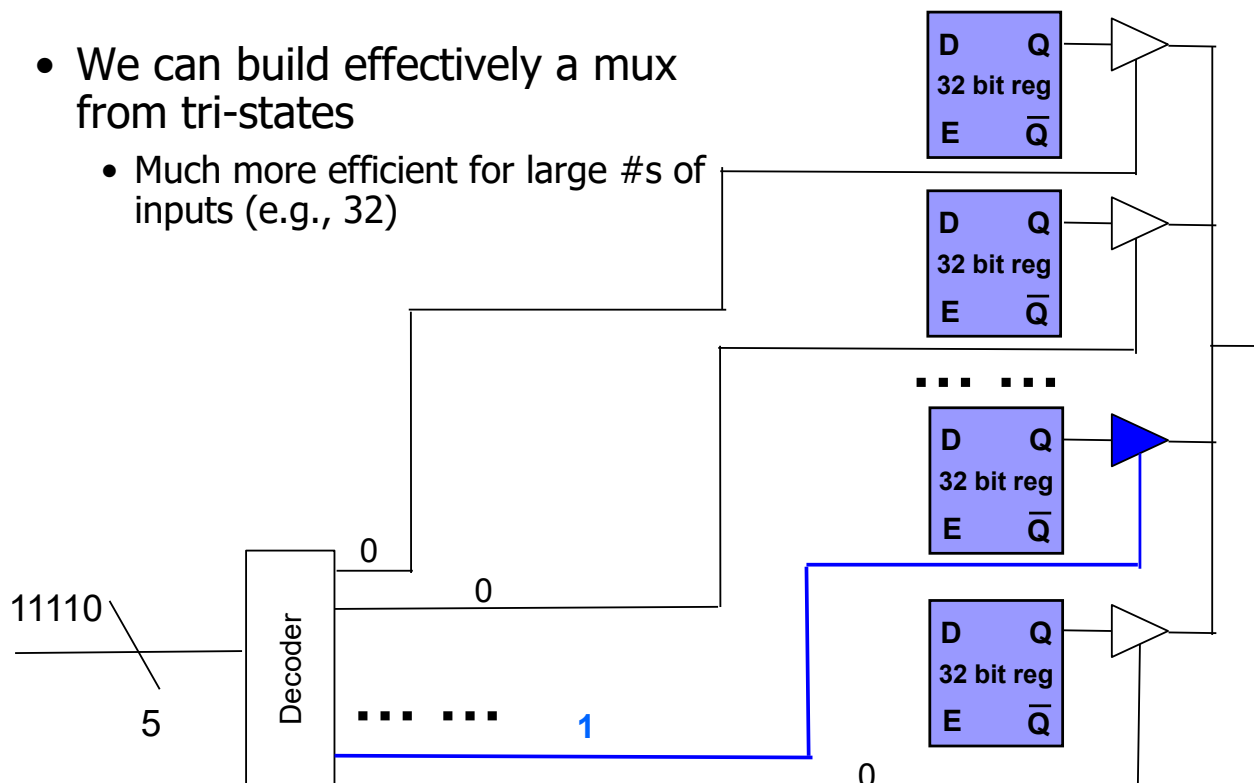
- We can build effectively a mux from tri-states
 - Much more efficient for large #s of inputs (e.g., 32)



28

Register File

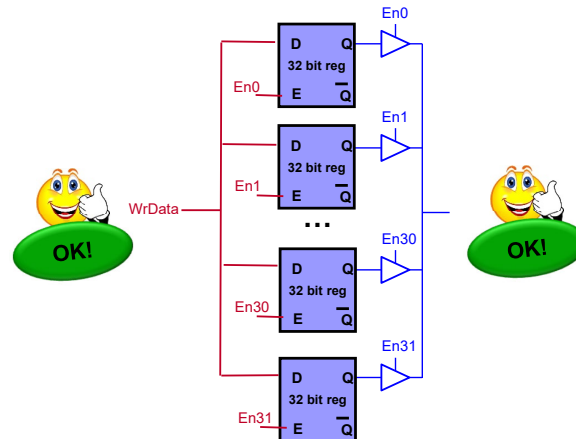- Now we can **write** and **read** in one clock cycle!



29

Ports

- What we just saw: **read** port
 - Ability to do one read / clock cycle
 - May want more: read 2 source registers per instr
 - Maybe even more if we do many instrs at once
 - This design: can just replicate port
 - Another decoder
 - Another set of tri-states
 - Another output bus (wire connecting the tri-states)
- Earlier: **write** port
 - Ability to do one write/cycle
 - Could add more: need muxes to pick wr values

30

Minor Detail

- FYI: This is not how a register file is implemented
 - (Though it is how other things are implemented)
 - Actually done with SRAM
 - We'll see how those work soon

31

Summary

Storage devices

D flip-flops

Registers

32