

ECE 550D

Fundamentals of Computer Systems and Engineering

Fall 2023

Storage and Clocking

Xin Li & Dawei Liu
Duke Kunshan University

Slides are derived from work by
Andrew Hilton, Tyler Bletsch and Rabi Younes (Duke)

Last time...

- Who can remind us what we did last time?
 - Add
 - Subtract
 - Bit shift
 - Floating point

So far...

- We can make logic to compute “math”
 - Add, subtract,... (we’ll see multiply/divide later)
 - Bitwise: AND, OR, NOT,...
 - Shifts
 - Selection (MUX)
 - ...pretty much anything
- But processors need state (hold value)
 - Registers
 - ...

3


Memory Elements

- All the circuits we looked at so far are **combinational circuits**: the output is a Boolean function of the inputs.
- We need circuits that can remember values (registers, memory)
- The output of the circuit is a function of the input **and** a function of a stored value (state)
- Circuits with storage are called **sequential circuits**
- Key to storage: feedback loops from outputs to inputs

4

Ideal Storage – Where We're Headed

 
- Ultimately, we want something that can hold 1 bit and we want to control when it is re-written





- However, instead of just giving it to you as a magic black box, we're going to first dig a bit into the box

5


 
Building up to the D Flip-Flop and beyond





SR Latch
(too awkward)

  

D Latch
(bad timing)

  



D Flip-Flop
(okay but only one bit)

  

Register
(nice!)

6

  FF Step #1: NOR-based Set-Reset (SR) Latch






R	S	Q
0	0	Q
0	1	1
1	0	0
1	1	—

Don't set both S & R to 1.
Seriously, don't do it.


7

Set-Reset Latch (Continued)

   


8

Set-Reset Latch (Continued)

 


9

Set-Reset Latch (Continued)

 

10


Set-Reset Latch (Continued)

 

11


SR Latch

 - Downside: S and R at once = chaos
- Downside: Bad interface
- So let's build on it to do better





12


 
Building up to the D Flip-Flop and beyond





SR Latch
(too awkward)

  

D Latch
(bad timing)

  


D Flip-Flop
(okay but only one bit)

  

Register
(nice!)


13

FF Step #2: Data Latch (“D Latch”)

 

Starting with SR Latch

Data Latch (D Latch)

 

Starting with SR Latch


Change interface to
Data + Enable (D + E)

If $E=0$, then $R=S=0$.


If $E=1$, then $S=D$ and $R=\neg D$

15

Data Latch (D Latch)

 


D	E	Q
0	1	0
1	1	1
-	0	Q

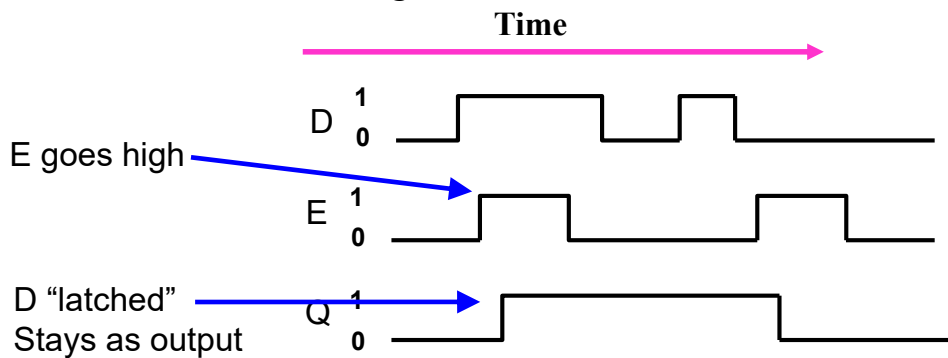


16

Data Latch (D Latch)

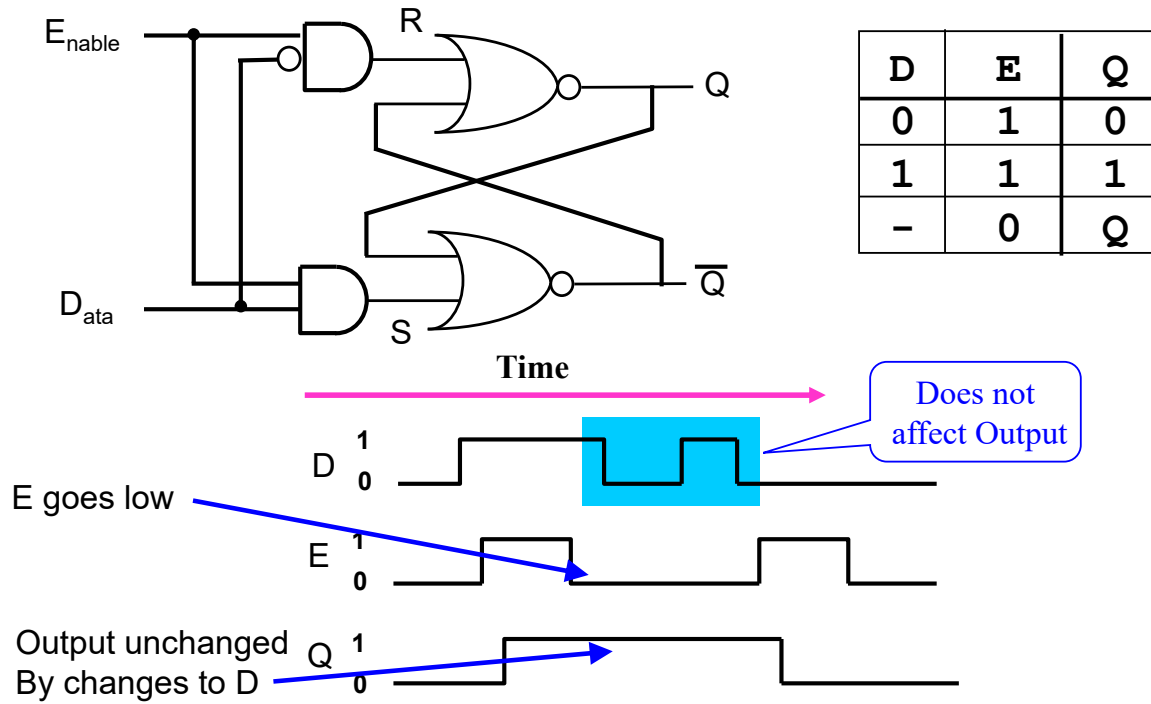


17

Data Latch (D Latch)

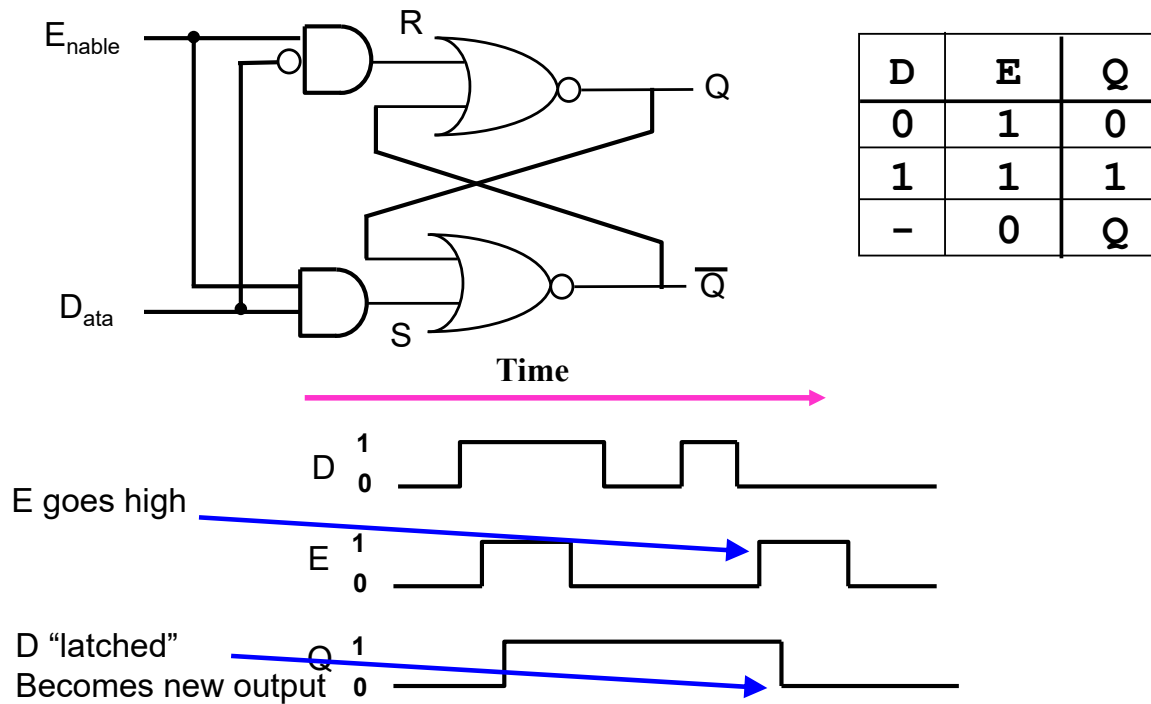

18

Data Latch (D Latch)

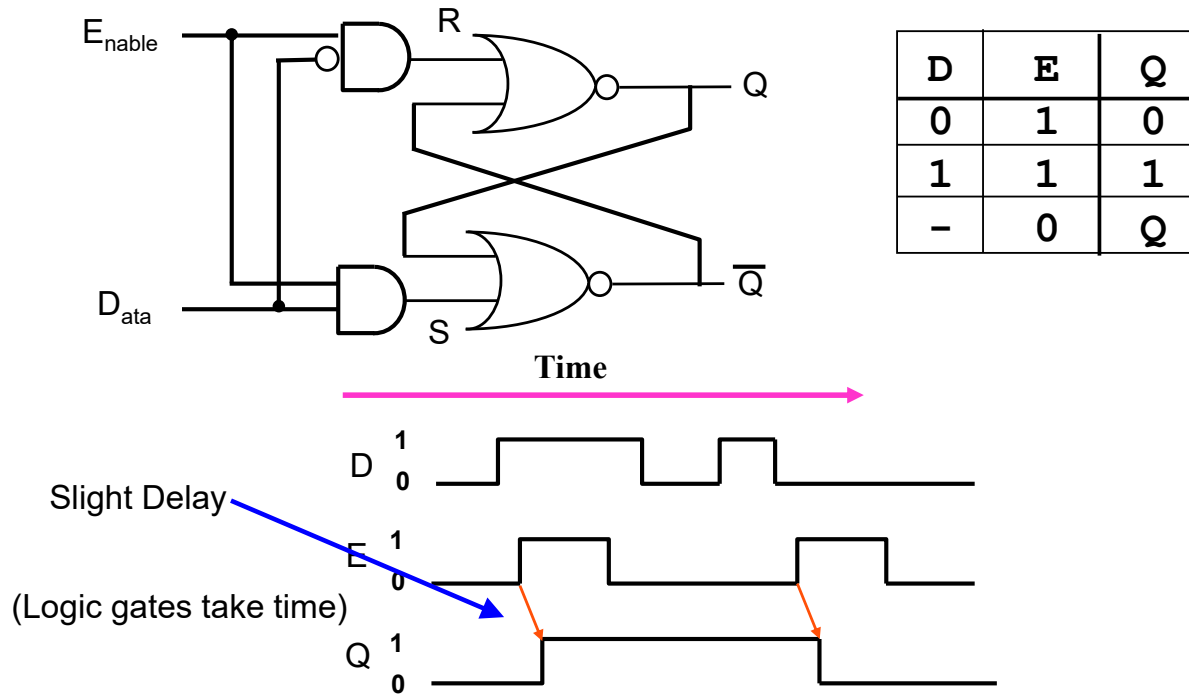

19


Logic Takes Time

- Logic takes time:
 - Gate delays: delay to switch each gate
 - Wire delays: delay for signal to travel down wire
 - Other factors (not going into them here)
- Need to make sure that signals timing is right
 - Don't want to have races or wacky conditions..

20

Clocks

 - Processors have a clock:
 - Alternates 0 1 0 1
 - Like the processor's internal metronome
 - Latch → logic → latch in one clock cycle




- 3.4 GHz processor = 3.4 Billion clock cycles/sec

21

FF Step #3: Using Level-Triggered D Latches

 
- First thoughts: Level Triggered
 - Latch enabled when clock is high
 - Hold value when clock is low



22

Strawman: Level Triggered

 - How we'd like this to work
 - Clock is low, all values stable




This slide describes how D-latches can malfunction because they were level triggered.
Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

23

Strawman: Level Triggered

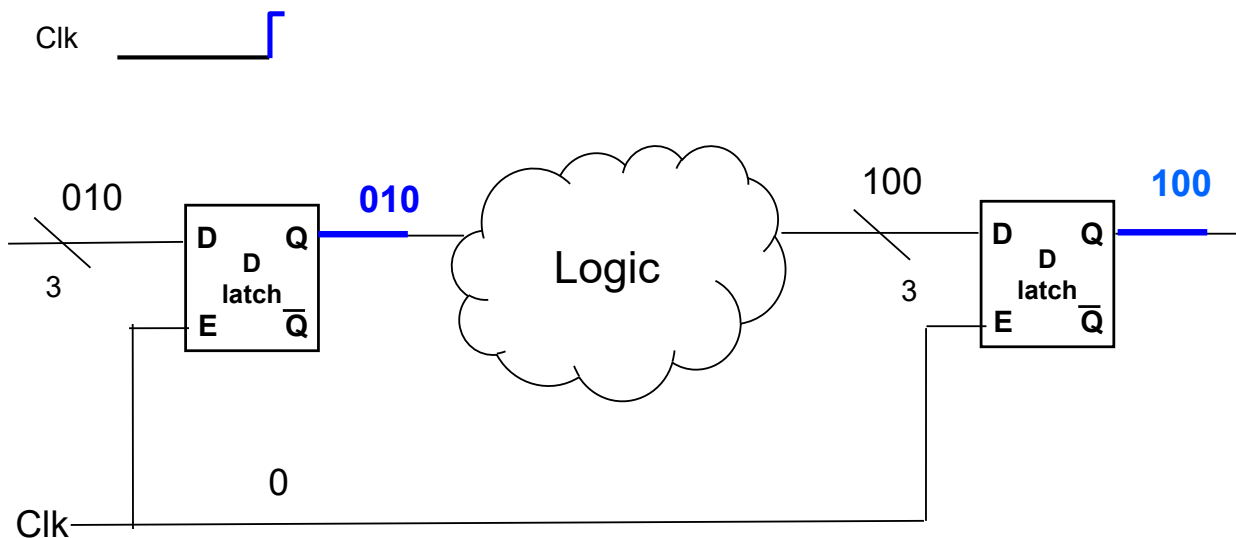- How we'd like this to work
 - Clock goes high and latches capture new values




This slide describes how D-latches can malfunction because they were level triggered.
Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

24

Strawman: Level Triggered

 - How we'd like this to work
 - Signals work their way through logic w/ high clk




This slide describes how D-latches can malfunction because they were level triggered. Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

25

Strawman: Level Triggered

 - How we'd like this to work
 - Clock goes low before signals reach next latch




This slide describes how D-latches can malfunction because they were level triggered. Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

26

Strawman: Level Triggered

 - How we'd like this to work
 - Clock goes low before signals reach next latch




This slide describes how D-latches can malfunction because they were level triggered. Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

27

Strawman: Level Triggered

 - How we'd like this to work
 - Everything stable before clk goes high




This slide describes how D-latches can malfunction because they were level triggered. Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

28

Strawman: Level Triggered

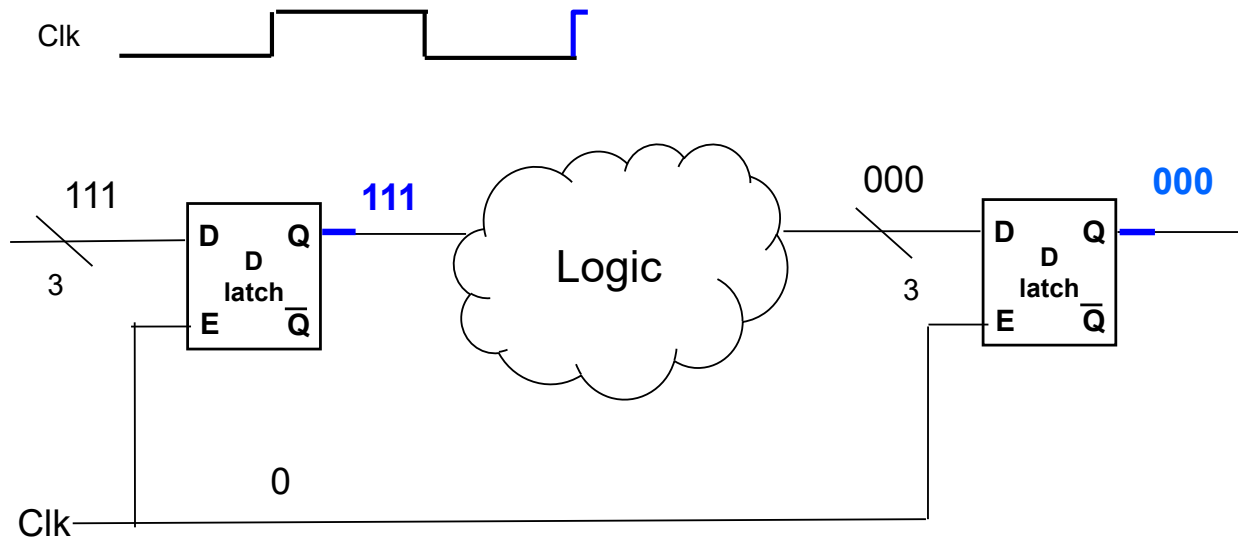- How we'd like this to work
 - Clk goes high again, repeat




This slide describes how D-latches can malfunction because they were level triggered.
Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

29

Strawman: Level Triggered

 - Problem: What if signal reaches latch too early?
 - I.e., while clk is still high




This slide describes how D-latches can malfunction because they were level triggered.
Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

30

Strawman: Level Triggered

 - Problem: What if signal reaches latch too early?
 - Signal goes right through latch, into next stage..




This slide describes how D-latches can malfunction because they were level triggered.
Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

31

That would be bad...

 
- Getting into a stage too early is bad
 - Something else is going on there → corrupted
 - Also may be a loop with one latch
- Consider incrementing counter (or PC)
 - Too fast: increment twice?





This slide describes how D-latches can malfunction because they were level triggered.
Real D-flip-flops are *edge-triggered*, and we're showing you *why* that's important.

32


 
Building up to the D Flip-Flop and beyond





SR Latch
(too awkward)

  

D Latch
(bad timing)

  

D Flip-Flop
(okay but only one bit)

  

Register
(nice!)

33

Summary

Can layout logic to compute things

Add, subtract,...

Now can store things

SR latch

D latch

Also understand clocks