

ECE 550DK

Fundamentals of Computer Systems and Engineering

Fall 2023

From Transistors to Gates

Xin Li & Dawei Liu
Duke Kunshan University

Slides are derived from work by
Andrew Hilton, Tyler Bletsch and Rabi Yunes (Duke)

Last time....

(Almost) every class will start with the same question:

- Who can remind us what we talked about last time?
(besides course policies)
- **Abstraction**
 - Interface vs Implementation

Power (Vcc) and Ground (Gnd)

Vcc 

Gnd 

- Two supply rails:
 - Power (aka Vcc, sometimes called Vdd) , e.g., +1.0 V
 - Logically, 1
 - Ground (Gnd, or Vss), e.g., 0 V
 - Logically, 0
 - Use Vcc/Gnd because that's what Quartus uses

3

Wires


Vcc 

Gnd 

- A wire (or other conductor) causes current to flow

4


Short circuit

 

- Short circuit: direct connection from power to ground
 - Very high current
 - Generates a lot of heat
 - Destroys your chip
 - Very bad!

5


Switching

 

- Suppose instead we had some sort of switch
 - Here, top connection conducts, connecting A to Vcc
 - The bottom half resists insulating A from Gnd

6


Switching

 

- If we switch our connection...
 - Current flows as A changes voltage levels
 - Connection to power is closed, so no short circuit

7

 
Transistors: Electrically controlled switches



- Two types:
 - NMOS (left: no circle):
 - Conducts when gate is 1, resists when gate is 0
 - PMOS (right: circle):
 - Conducts when gate is 0, resists when gate is 1

8

CMOS: Complementary MOS

 


- CMOS (most common, all we care about):
 - Put PMOS and NMOS in complementary fashion
 - Either PMOS conducts or NMOS conducts, but not both
- Form a logic gate
 - Input (s): connected to gates of transistors
 - Output: connected to drains

CMOS = "Complementary Metal Oxide Semiconductor"

9


CMOS: Complementary MOS

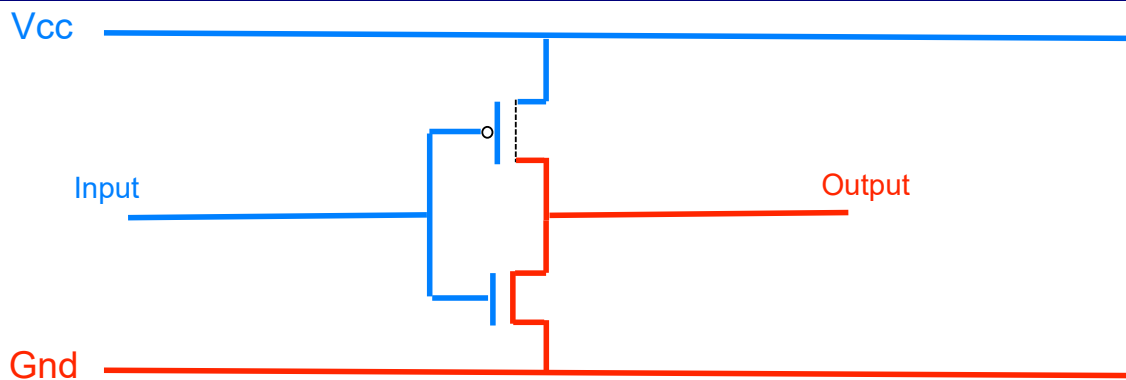

- Let's see how this works.
 - Suppose Input = 1 (circuitry to control input, not shown)
 - PMOS transistor resists
 - No connection between Output and Vcc
 - NMOS transistor conducts
 - Connection between Output and Gnd
 - Output is 0

10

CMOS: Complementary MOS

 

- Now suppose Input changes to 0
 - PMOS transistor conducts
 - Connection between Output and Vcc
 - NMOS transistor conducts
 - No Connection between Output and Gnd
 - Output is 1


11

Switching delays

- Note: this doesn't happen instantly
 - There is some delay as these change
 - Factors that affect the delay
 - Voltage
 - Higher voltage = faster switching, but more power/energy
 - Resistance
 - Lower resistance = faster switching
 - Capacitance
 - Lower capacitance = faster switching
 - Calculating delay = hard, so we let our tools do it

12


CMOS: Complementary MOS

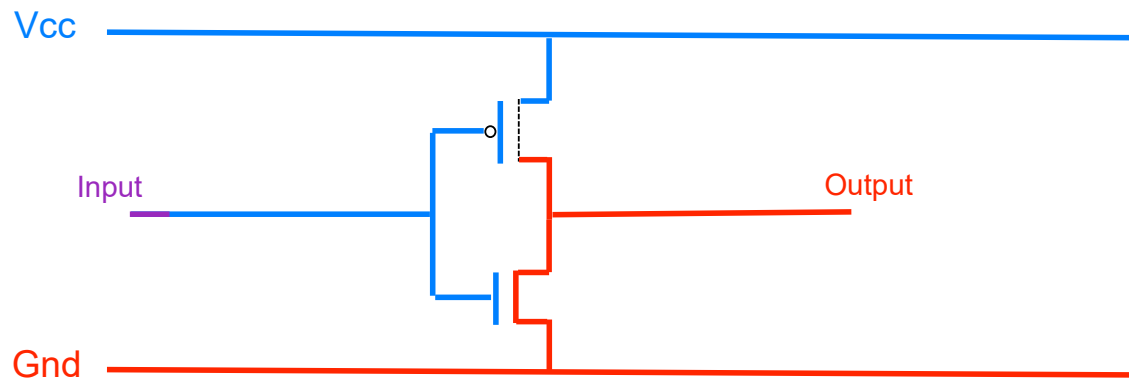

- Slightly more accurate with respect to time
 - Input starts to swing from 1 to 0 (not instant)

13


CMOS: Complementary MOS

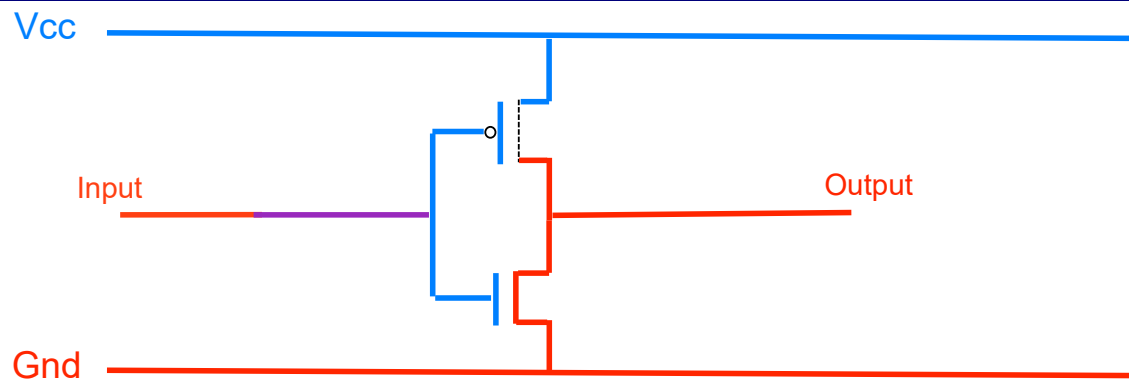

- Slightly more accurate with respect to time
 - Input starts to swing from 1 to 0 (not instant)
 - Change propagates along wires (also takes time)

14


CMOS: Complementary MOS

 

- Slightly more accurate with respect to time
 - Input starts to swing from 1 to 0 (not instant)
 - Change propagates along wires (also takes time)
 - Transistors start to switch (partially conductive)

15


CMOS: Complementary MOS

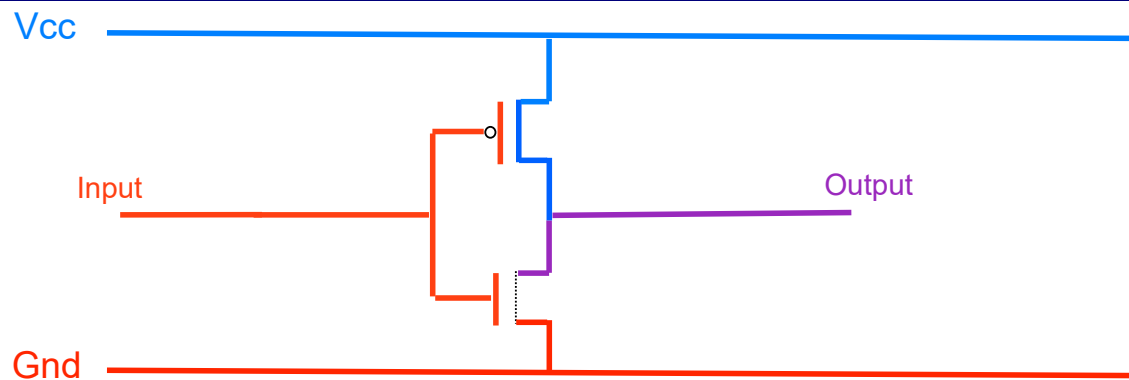

- Slightly more accurate with respect to time
 - Input starts to swing from 1 to 0 (not instant)
 - Change propagates along wires (also takes time)
 - Transistors start to switch (partially conductive)
 - Inputs reach 0 (sometime)
 - Transistors fully open/closed
 - Output may take time to transition

16


CMOS: Complementary MOS

 

- Slightly more accurate with respect to time
 - Input starts to swing from 1 to 0 (not instant)
 - Change propagates along wires (also takes time)
 - Transistors start to switch (partially conductive)
 - Inputs reach 0 (sometime)
 - Transistors fully open/closed
 - Output may take time to transition

17

Our first logic gate: The inverter

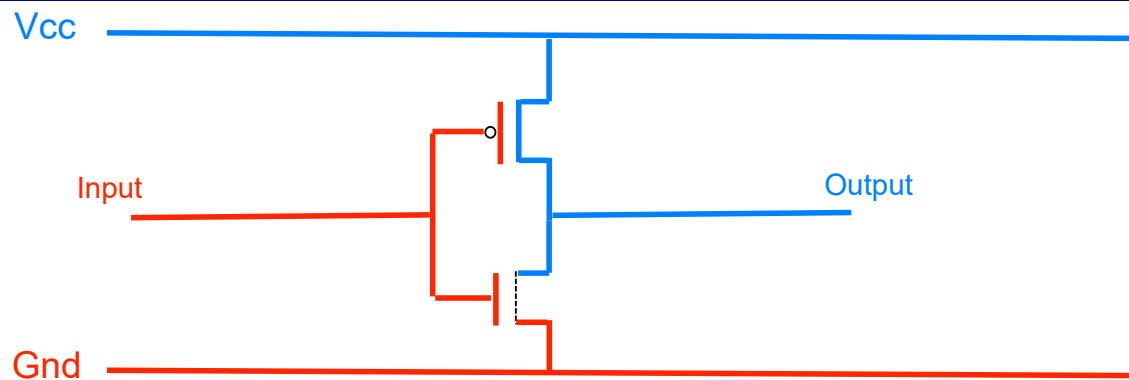


- This circuit is a logic gate: inverter or “NOT gate”
 - Gives logical negation of its input
 - Input = 0, Output = 1
 - Input = 1, Output = 0
 - Typically, just draw the gate, instead of the transistors:



18

Our first logic gate: The inverter

 

- (Small) Example of abstraction
 - Interface: “do logical negation”
 - Implementation: how to hook up the transistors



19

Let's build a more interesting gate

- Next, let us build a 2-input NOR gate
 - Here is a **truth table** for NOR
 - Shows output values for all possible inputs
 - Output = 1 when A and B = 0
 - Connect PMOS in **series**
 - (Not A) and (Not B)
 - Output = 0 when A or B = 1
 - Connect NMOS in **parallel**
 - Not (A or B)


A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

Note: two formulas are logically equivalent (DeMorgan's Laws)

- PMOS formula has NOTs on inputs
- NMOS formula has NOT on output

20


The NOR gate

 

- NOR Gate
 - PMOS in series (both A and B must be 0 to get 1)
 - NMOS in parallel (either A or B at 1 results in 0)
- Side note: real chips have several layers to route wires
 - 3D drawing is hard, just label inputs

21


The NOR gate

 

- NOR Gate
 - Same gate, just changed B's value to 1
 - Now output = 0
 - PMOS connected to B resists, blocking connection to V_{cc}
 - NMOS connected to B conducts, forming connection go Gnd


22

The NOR gate

 

- NOR Gate

 - Same gate, now change A to 1
- Output stays at 0
- Two connections to Gnd, but that's fine



23


Let's build a more interesting gate

- I'll let you all try a 2-input NAND gate
 - Here is a **truth table** for NAND

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0


24

The NAND Gate

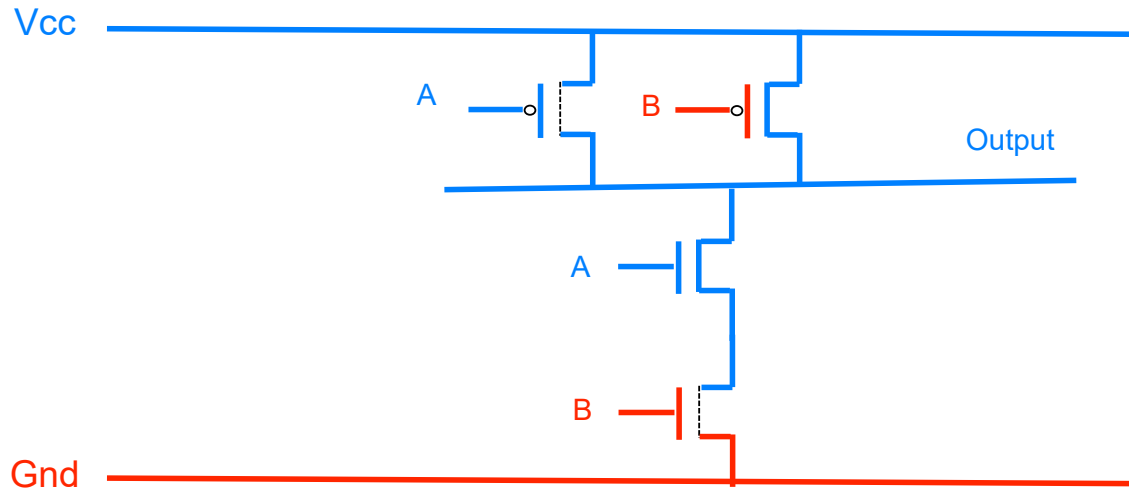

- The NAND Gate







 
- PMOS in parallel (either at 0 results in a 1)
- NMOS in series (both at 1 results in 0)



25

Boolean Gates

       - Actually a bunch of standard logic gates:




How to keep them all straight?


26

Guide to Remembering your Gates

 - This one looks like it just points its input where to go
 - It just produces its input as its output
 - Called a buffer



- A circle always means negate (invert)

 

Circle = NOT

27


Guide to Remembering your Gates



Straight like an A




Curved, like an O

 


XOR looks like OR (curved line), but has two lines (like an X does)

Circle means NOT

 

(XNOR is 1-bit "equals" by the way)

 

28

Next Time...

- Next time, we'll delve into Combinatorial Logic
 - Putting gates together to do useful things