

ECE 550D

Fundamentals of Computer Systems and Engineering

Fall 2023

Datapaths

Xin Li & Dawei Liu
Duke Kunshan University

Slides are derived from work by
Andrew Hilton, Tyler Bletsch and Rabih Younes (Duke)

Last time

- What did we do last time?
 - MIPS Assembly


Now confluence of MIPS + digital logic

- Start of semester: Digital Logic
 - Building blocks of digital design
- Most recently: MIPS assembly, ISA
 - Lowest level software
- Now: where they meet...
 - Datapaths: hardware implementation of processors


Necessary ingredient: the ALU

- **ALU: Arithmetic/Logic Unit**

 
- Performs any supported math or logic operation on two inputs
- Which operation is chosen by a third input



Add/Subtract With Overflow Detection

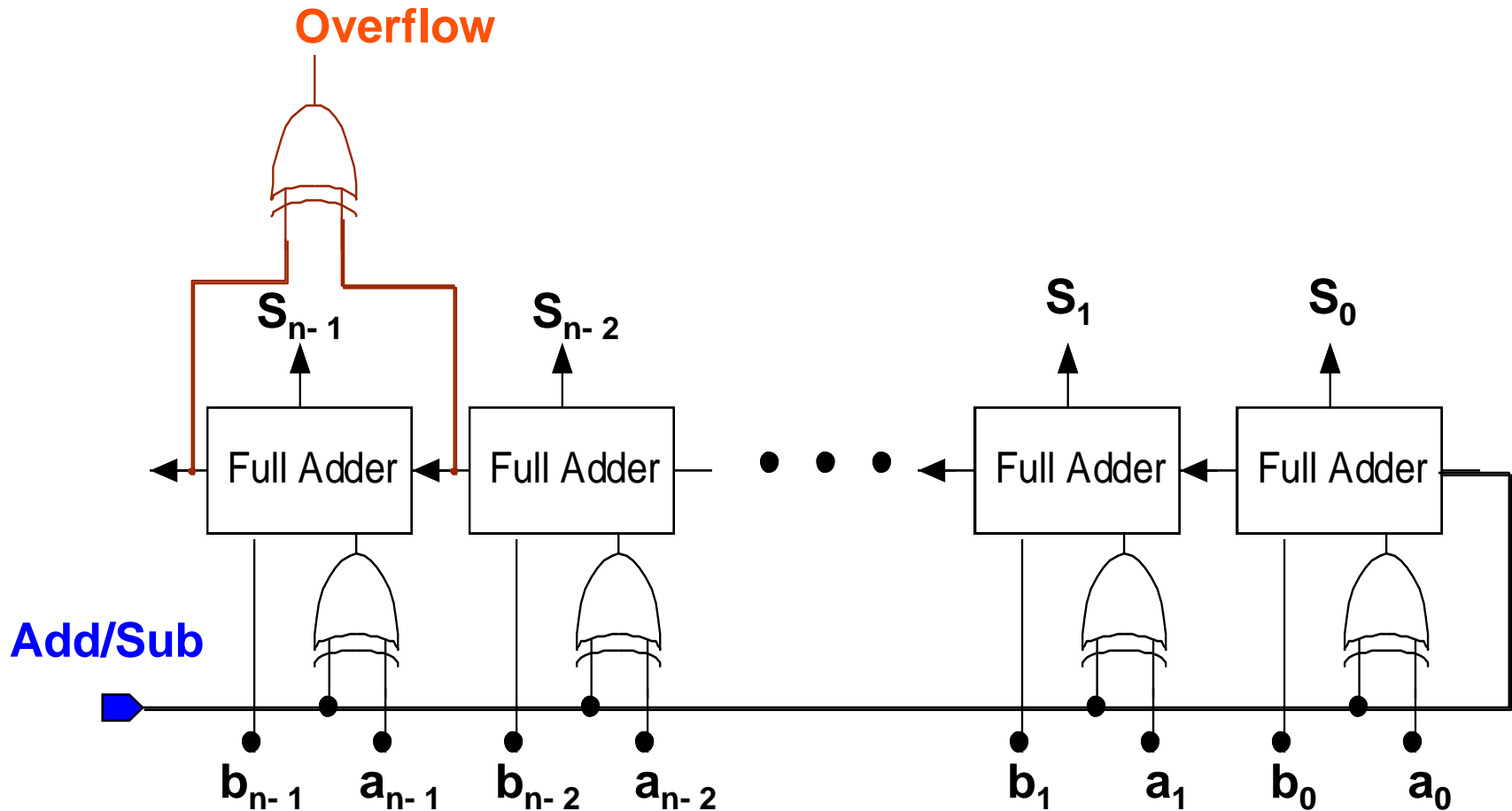


ALU Slice

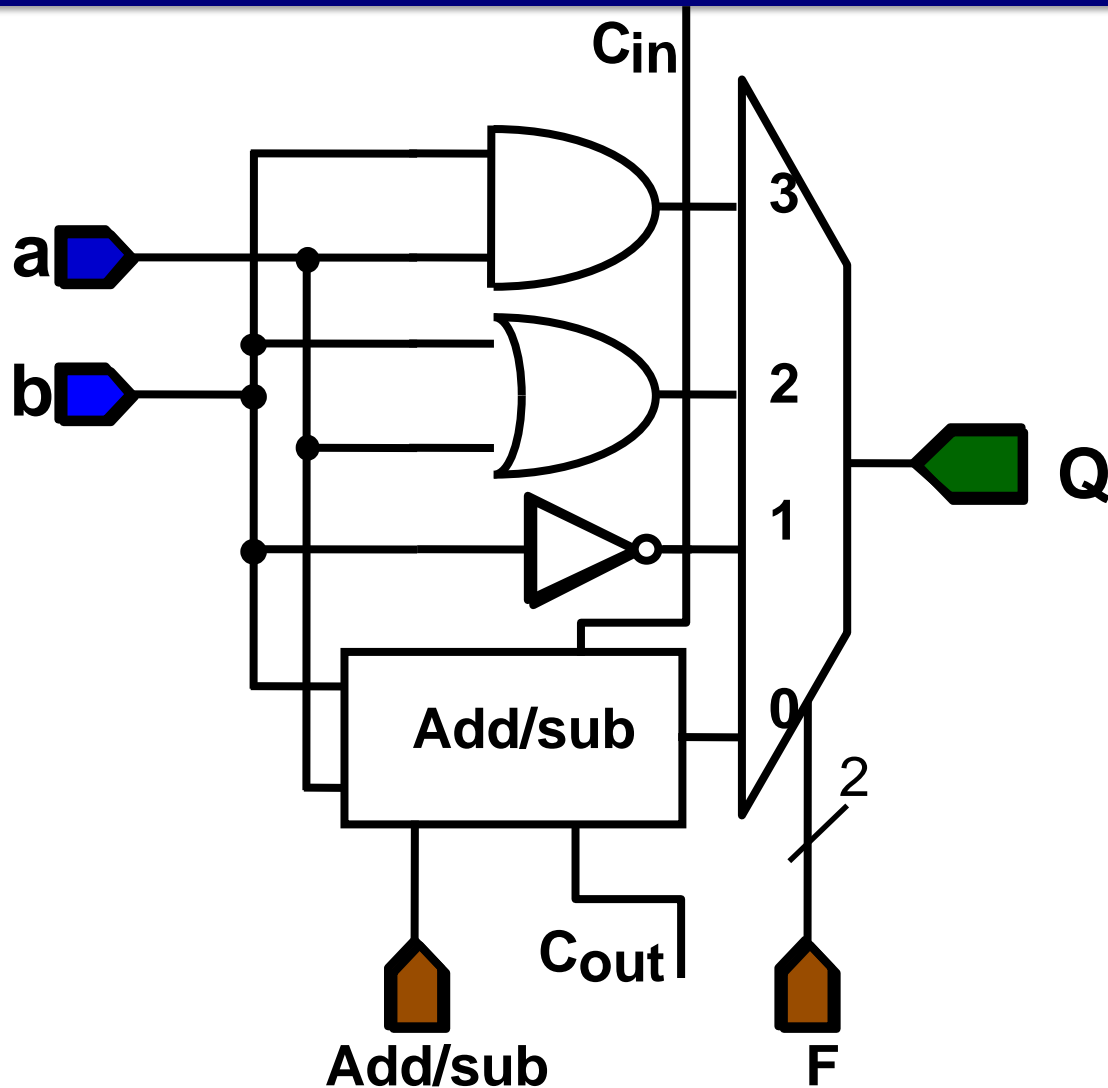

A	F	Q
0	0	$a + b$
1	0	$a - b$
-	1	NOT b
-	2	a OR b
-	3	a AND b

The ALU

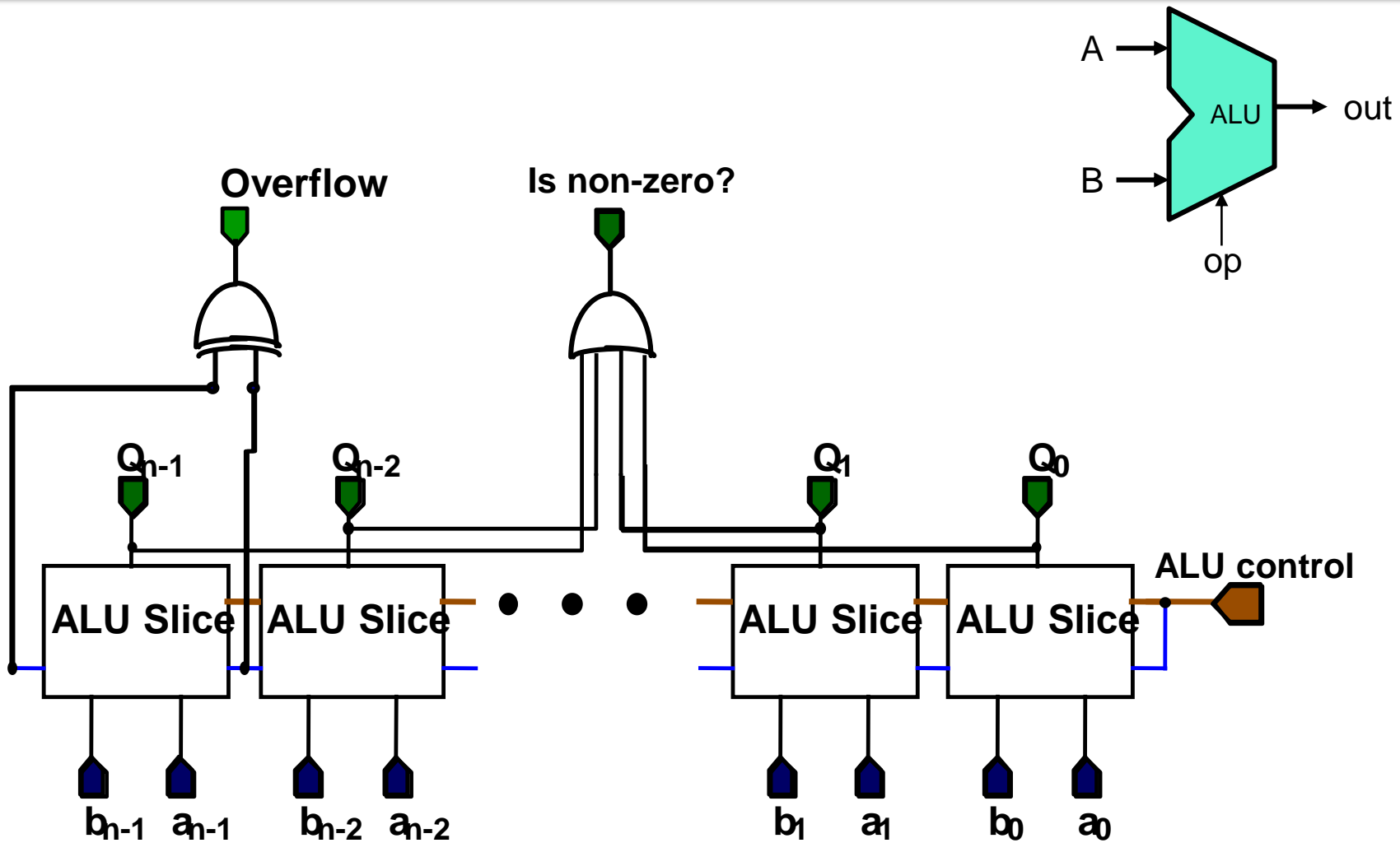

Datapath for MIPS ISA

- Consider only the following instructions

`add $1,$2,$3`

`addi $1,2,$3`

`lw $1,4($3)`


`sw $1,4($3)`

`beq $1,$2,PC_relative_target`

`j absolute_target`


- Why only these?
 - Most other instructions are the same from datapath viewpoint
 - The one's that aren't are left for you to figure out

Remember The von Neumann Model?

 


- **Instruction Fetch:**
Read instruction bits from memory
- **Decode:**
Figure out what those bits mean
- **Operand Fetch:**
Read registers (+ mem to get sources)
- **Execute:**
Do the actual operation (e.g., add the #s)
- **Result Store:**
Write result to register or memory
- **Next Instruction:**
Figure out mem addr of next insn, repeat

Start With Fetch

 

- Same for all instructions (don't know insn yet)
- PC and instruction memory
- A +4 incrementer computes default next instruction PC
 - Details of Insn Mem: later...
 - For now: just assume a bunch of DFFs


First Instruction: add

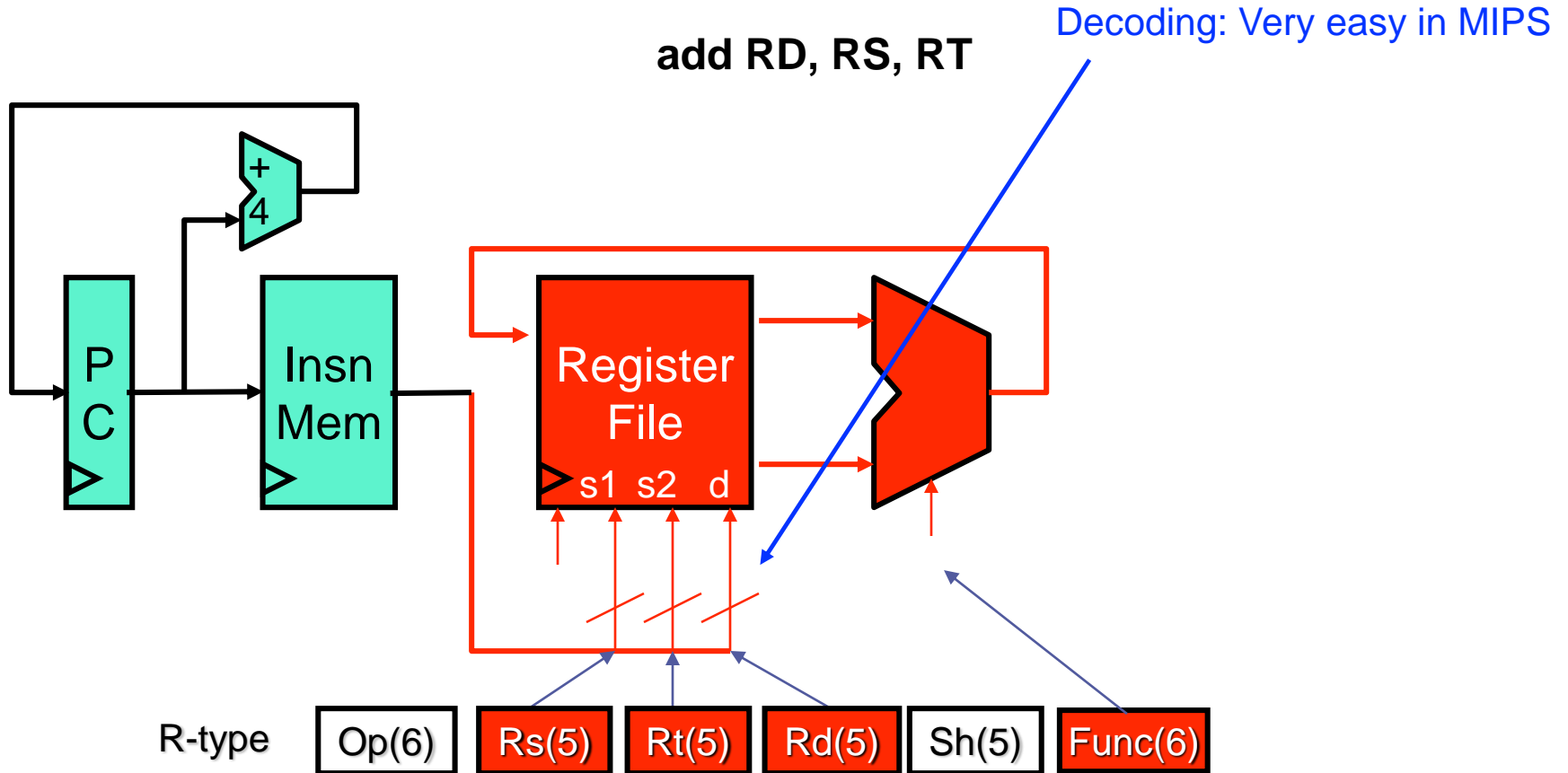

- Add register file and ALU

Second Instruction: addi


addi RT, RS, const16

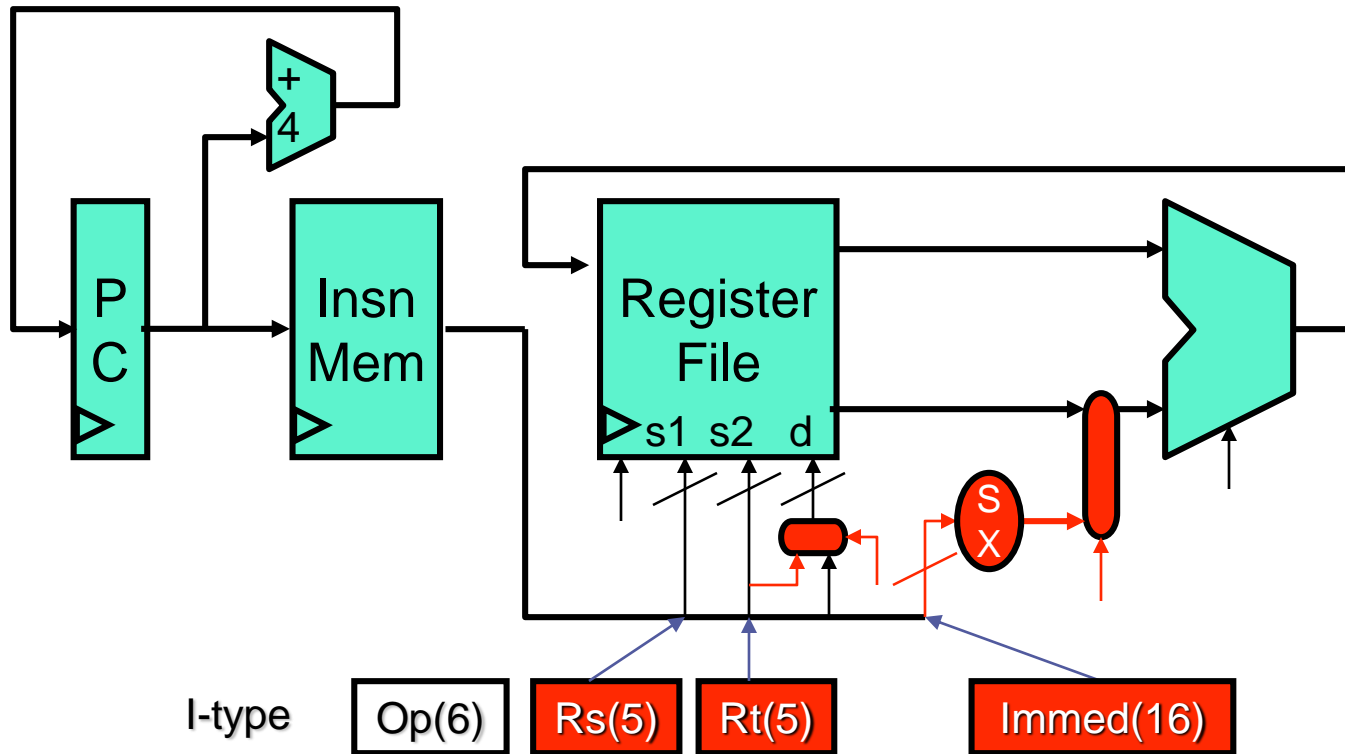

- Destination register can now be either Rd or Rt
- Add sign extension unit and mux into second ALU input

Third Instruction: lw


lw RT, off16(RS)

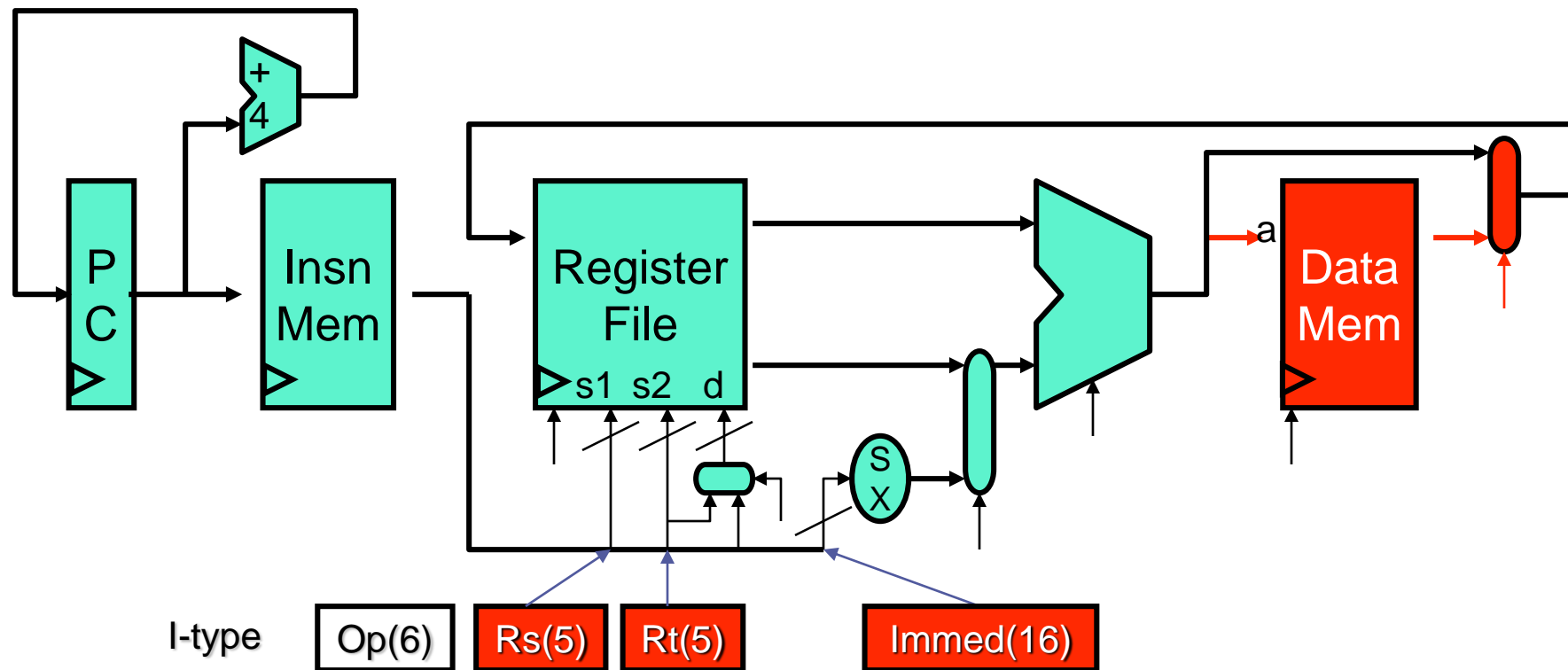

- Add data memory, address is ALU output
- Add register write data mux to select memory output or ALU output


Fourth Instruction: sw

sw RT, off16(RS)

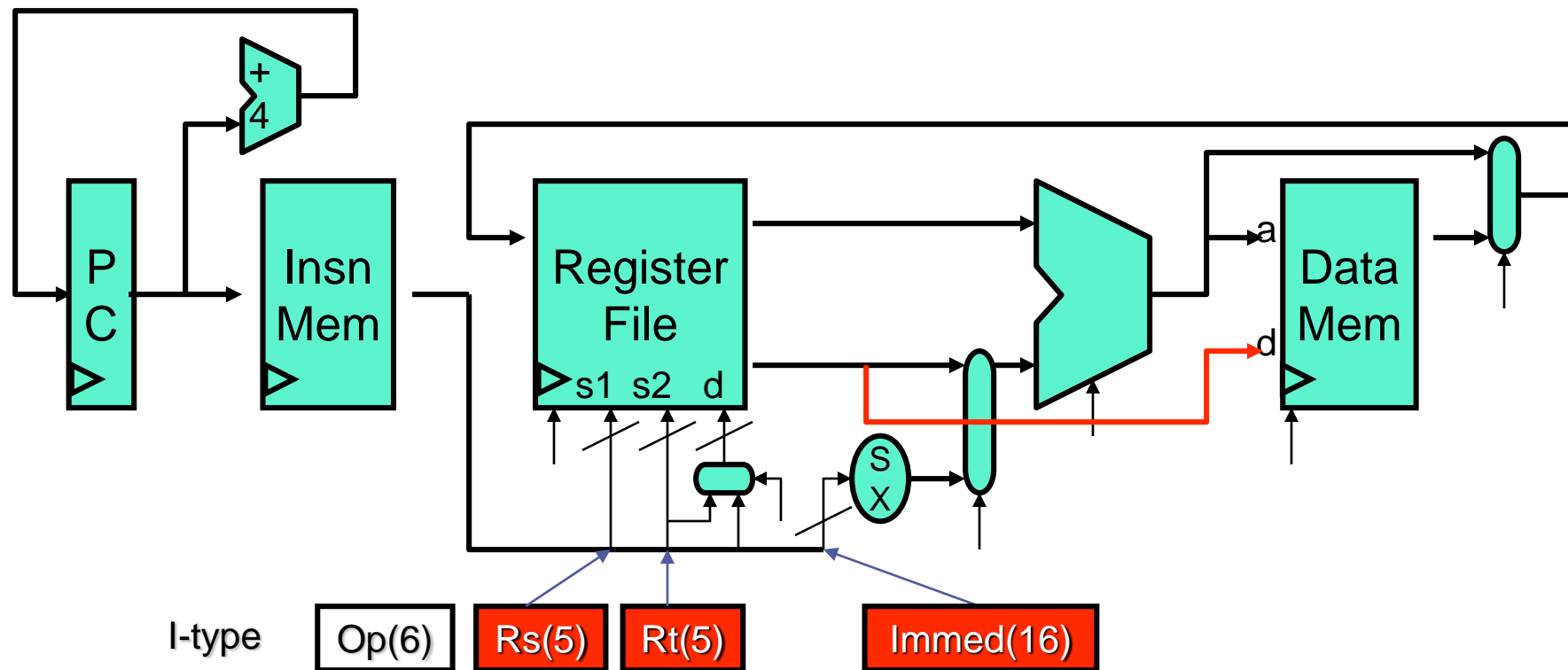


- Add path from second input register to data memory data input

Fifth Instruction: beq

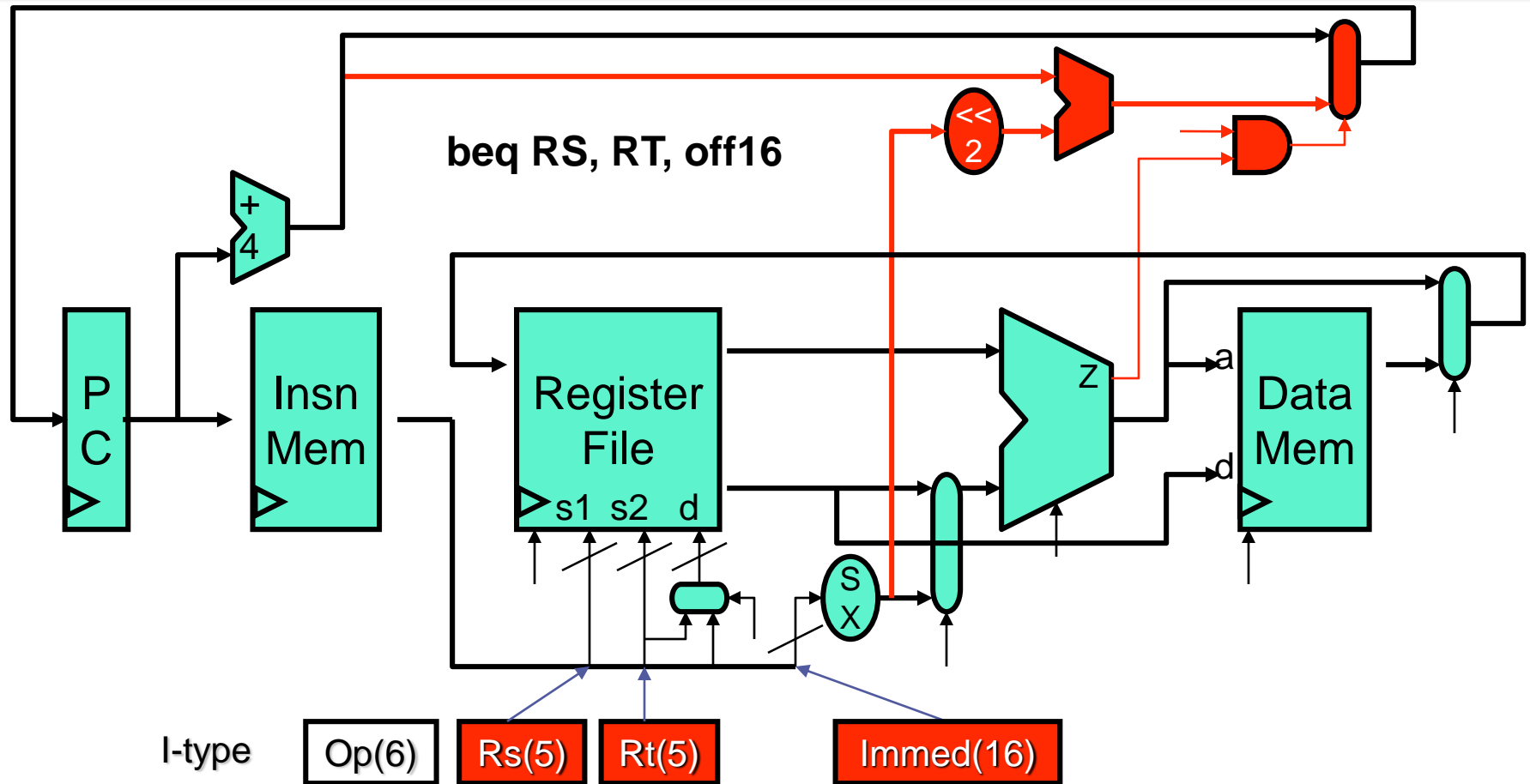


- Add left shift unit and adder to compute PC-relative branch target
- Add PC input mux to select PC+4 or branch target
 - Note: shift by fixed amount very simple

Sixth Instruction: j

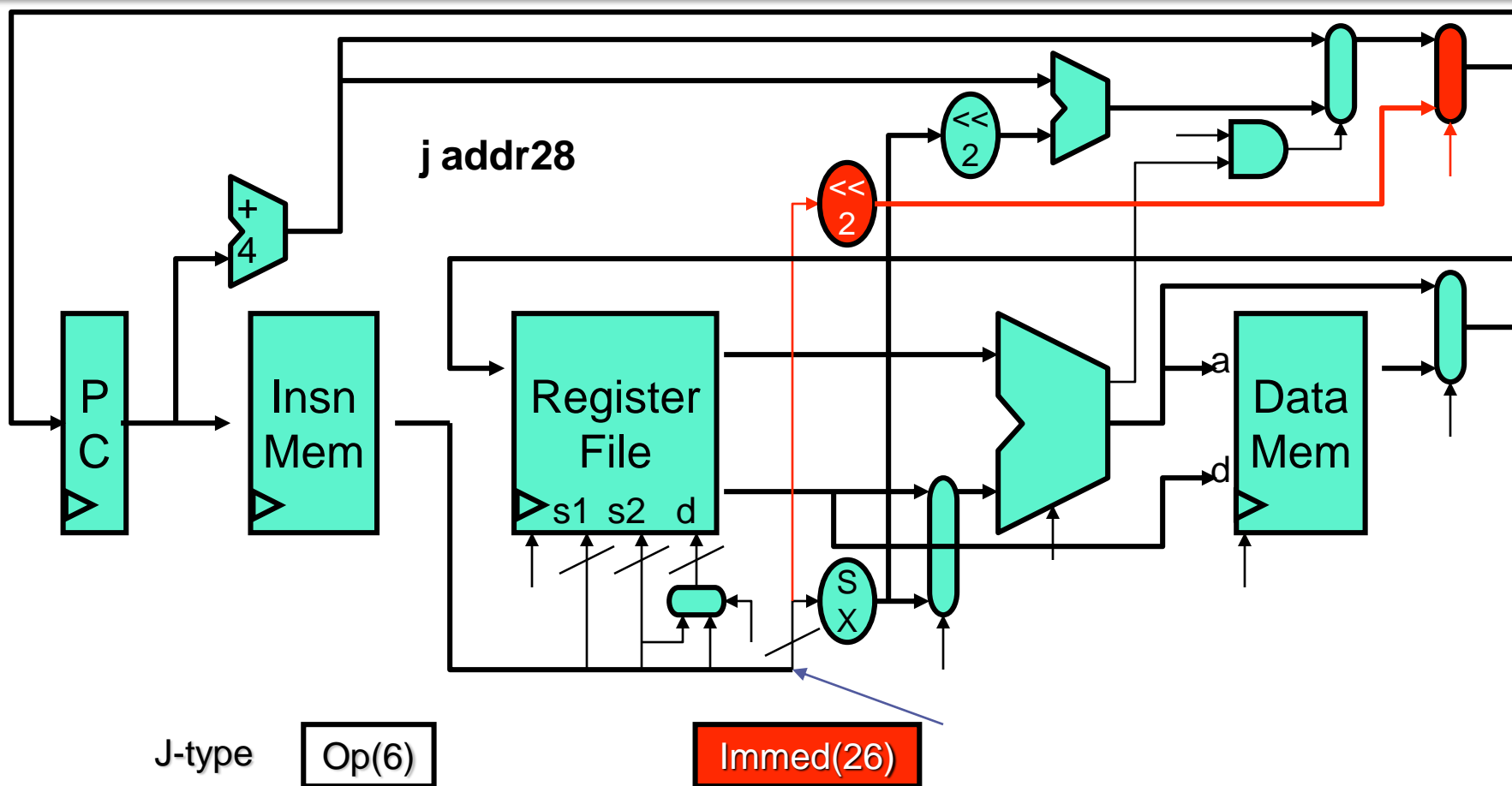


- Add shifter to compute left shift of 26-bit immediate
- Add additional PC input mux for jump target

More Instructions...

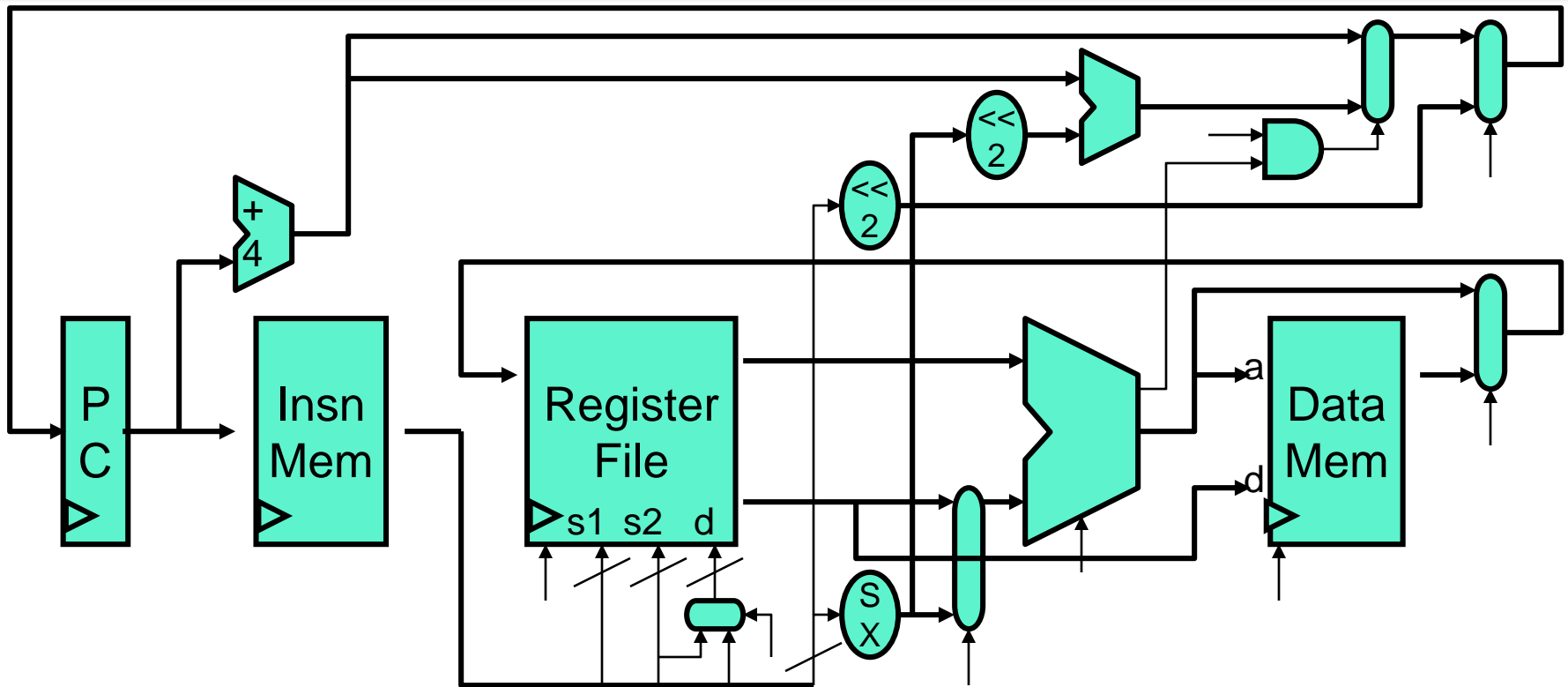


- Figure out datapath modifications for
 - jal (J-type)
 - jr (R-type)

Jal

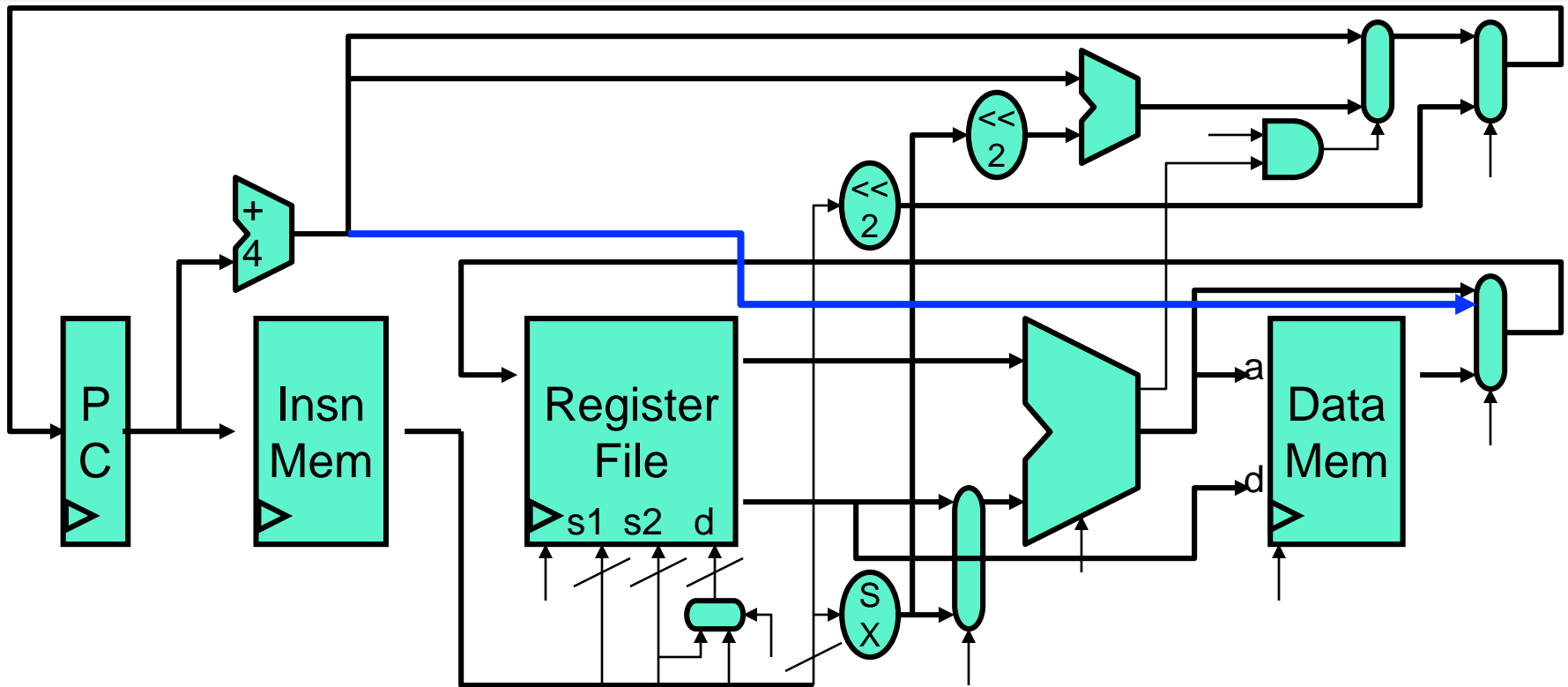


- For jal, need to get PC+4 to RF write mux

JR

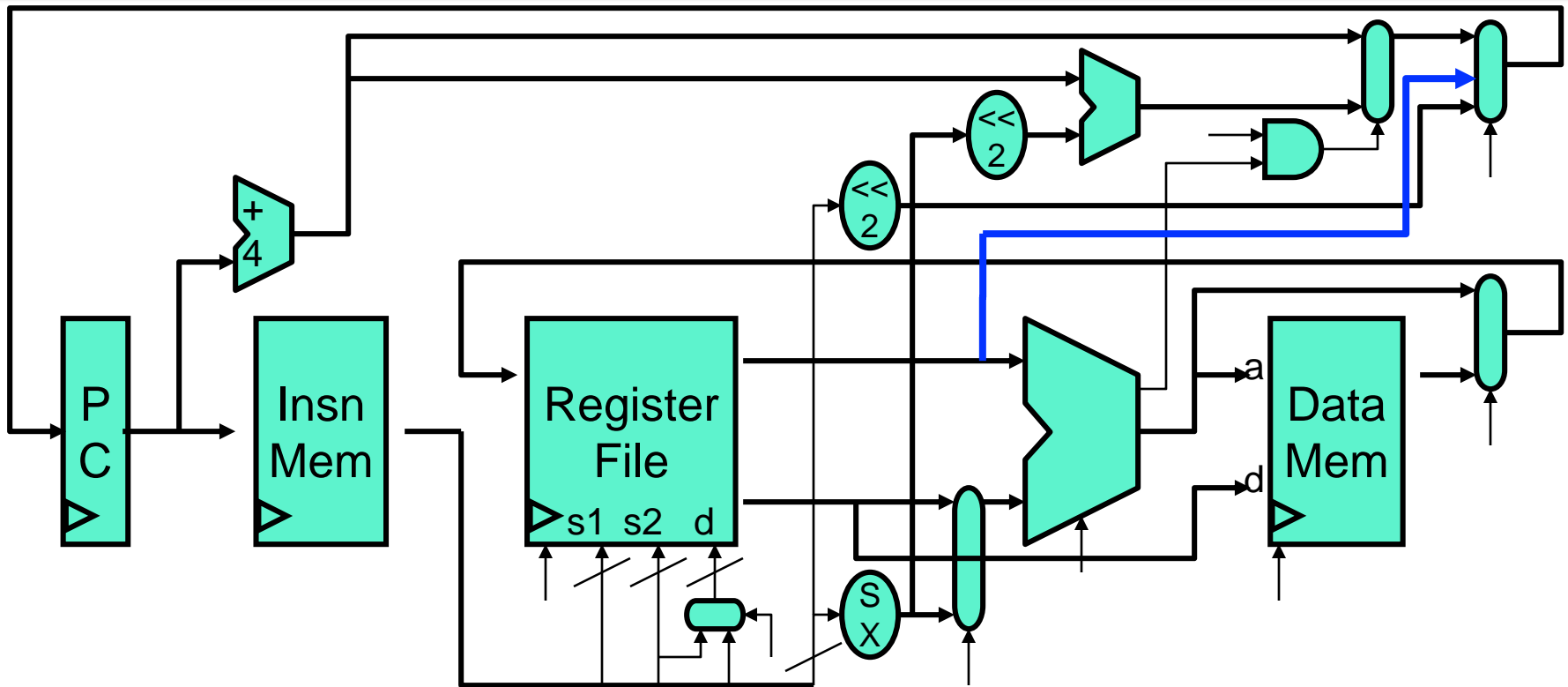


- For JR need to get RF read value to next PC mux

Good practice: Try other insns

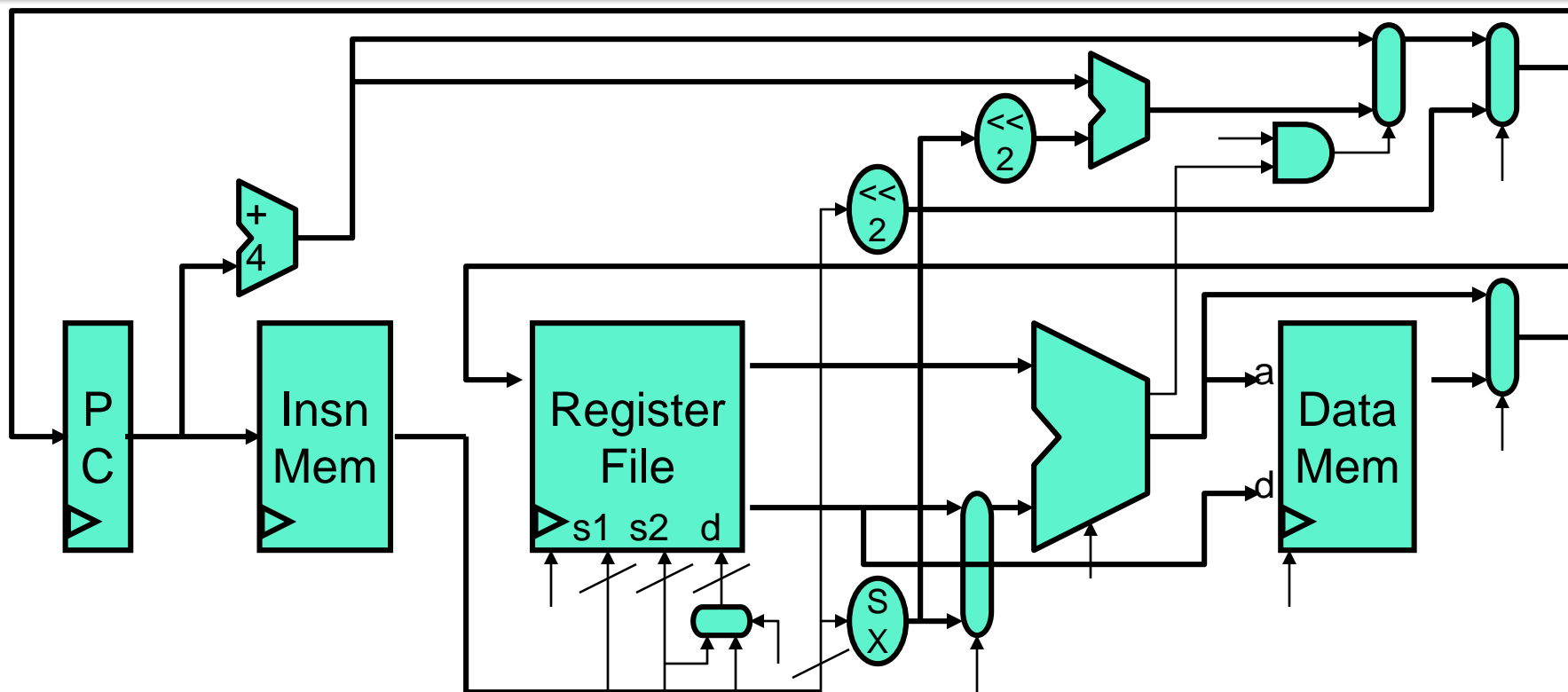


- Pick other MIPS instructions, contemplate how to add them

What Is Control?

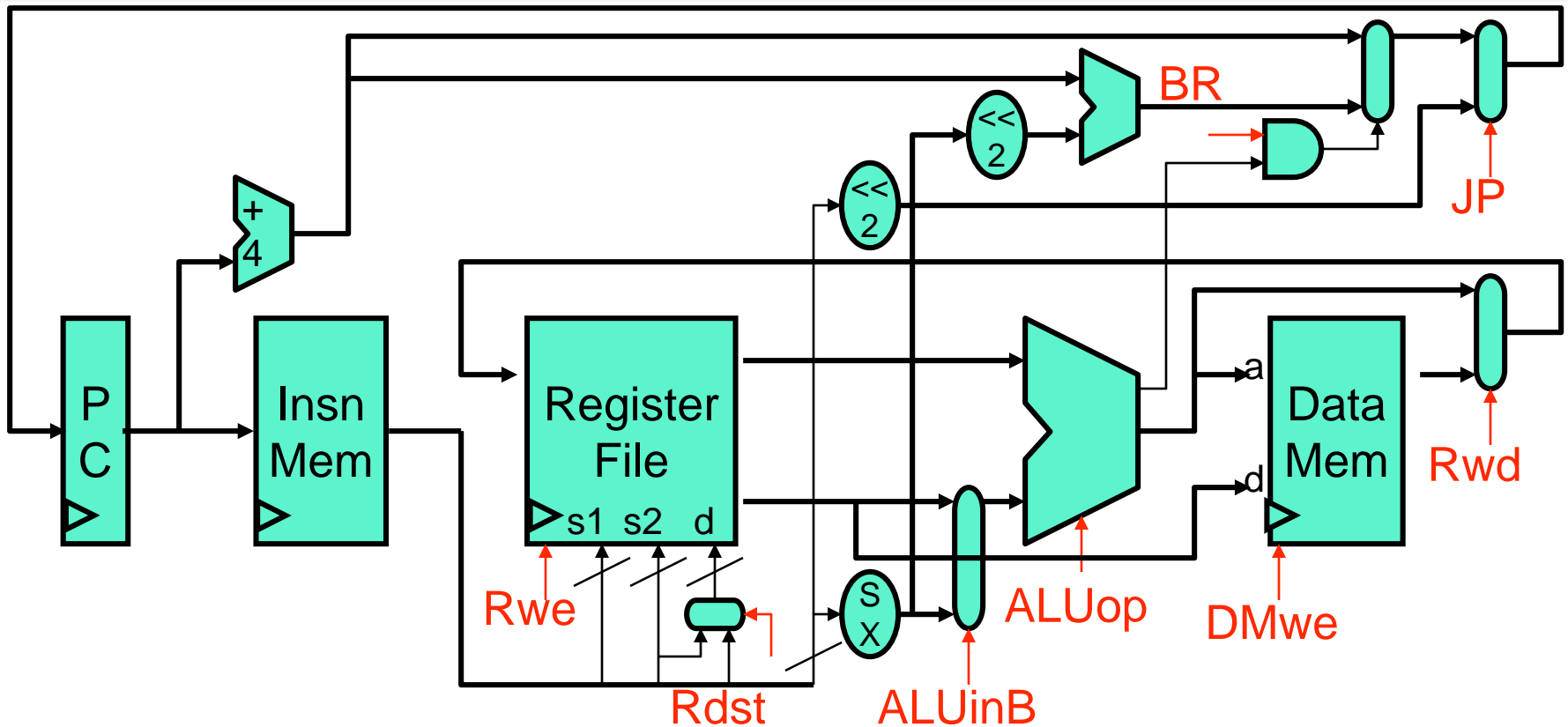


- 8 signals control flow of data through this datapath
 - MUX selectors, or register/memory write enable signals
 - A real datapath has 300-500 control signals

Example: Control for add

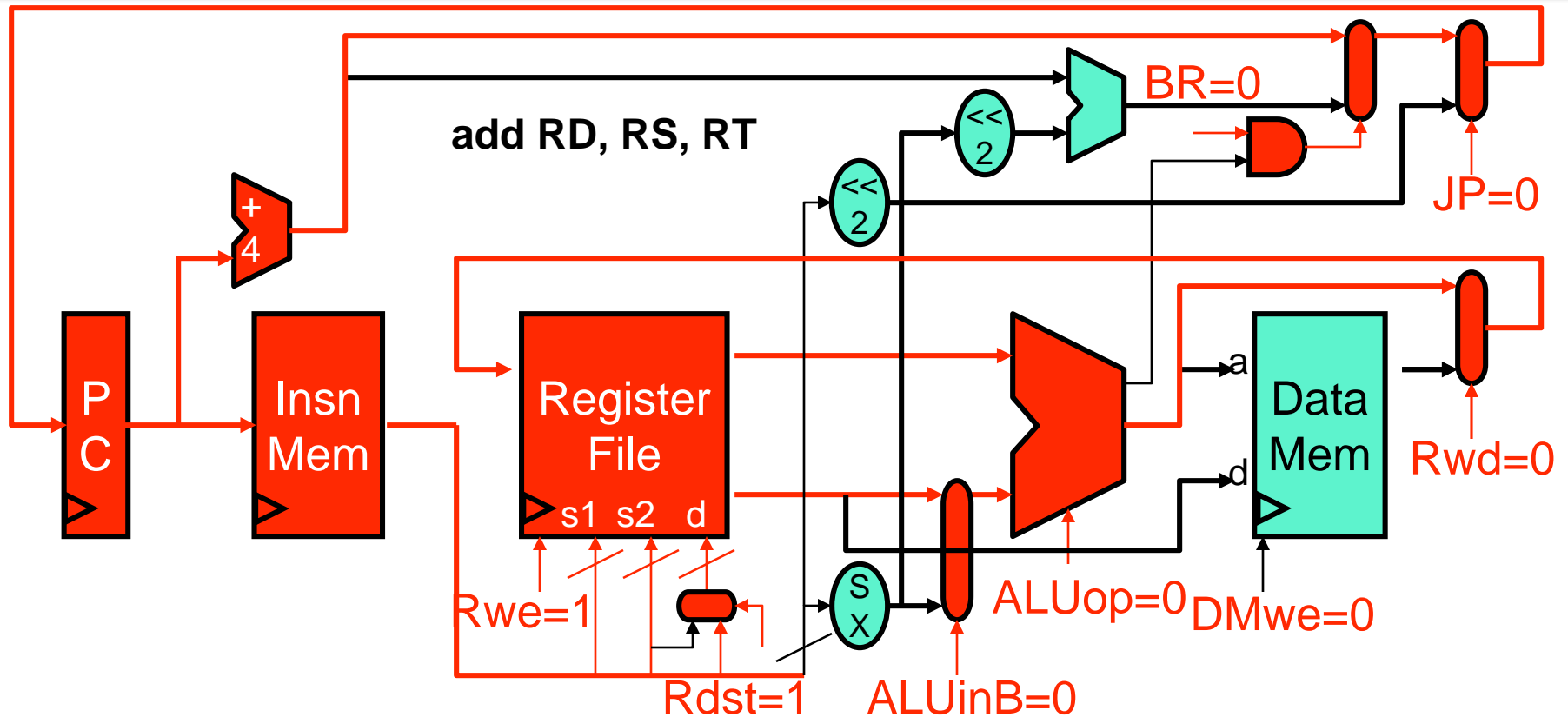


- Control for an instruction:
 - Values of all control signals to correctly execute it

Example: Control for sw

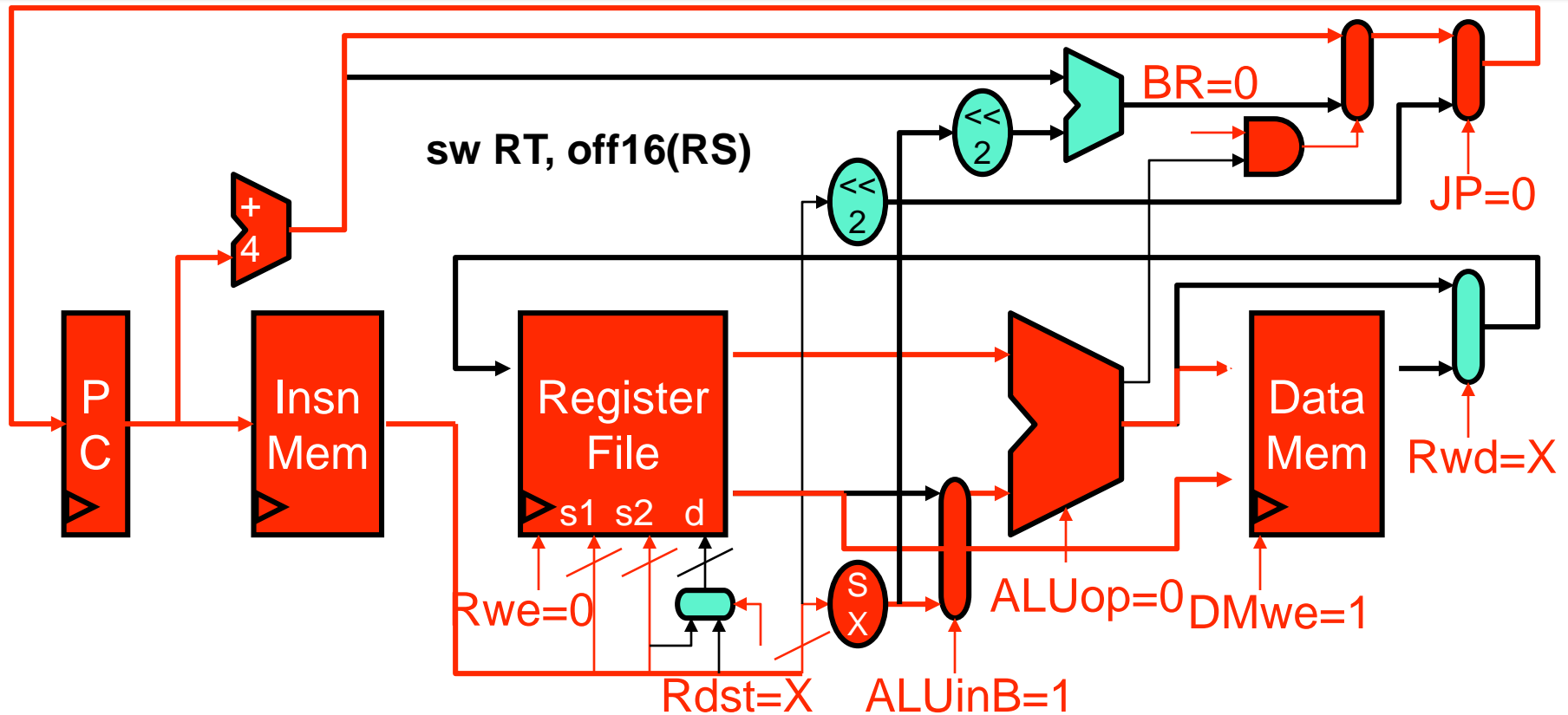


- Difference between **sw** and **add** is 5 signals
 - 3 if you don't count the X (don't care) signals

Example: Control for beq

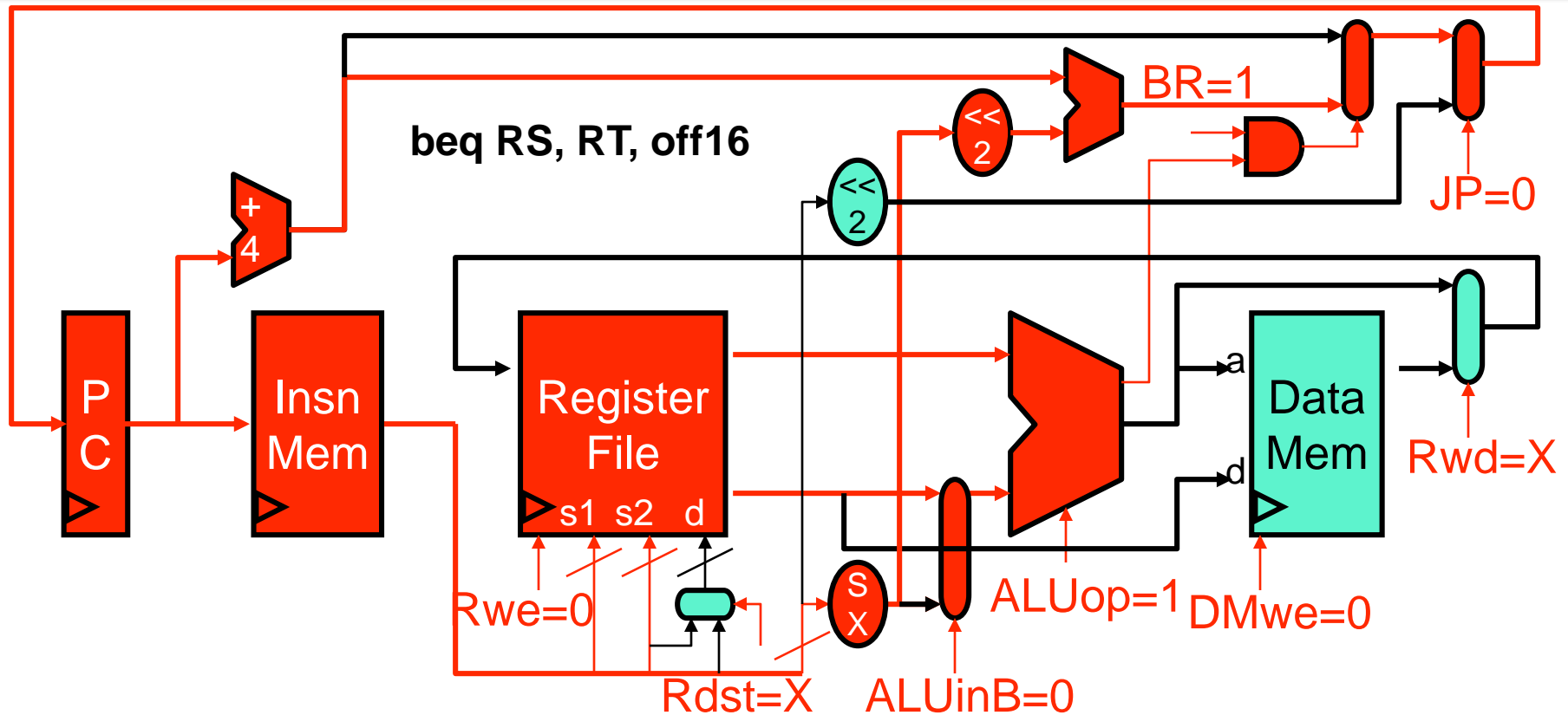


- Difference between **sw** and **beq** is only 4 signals

Example: Control for LW

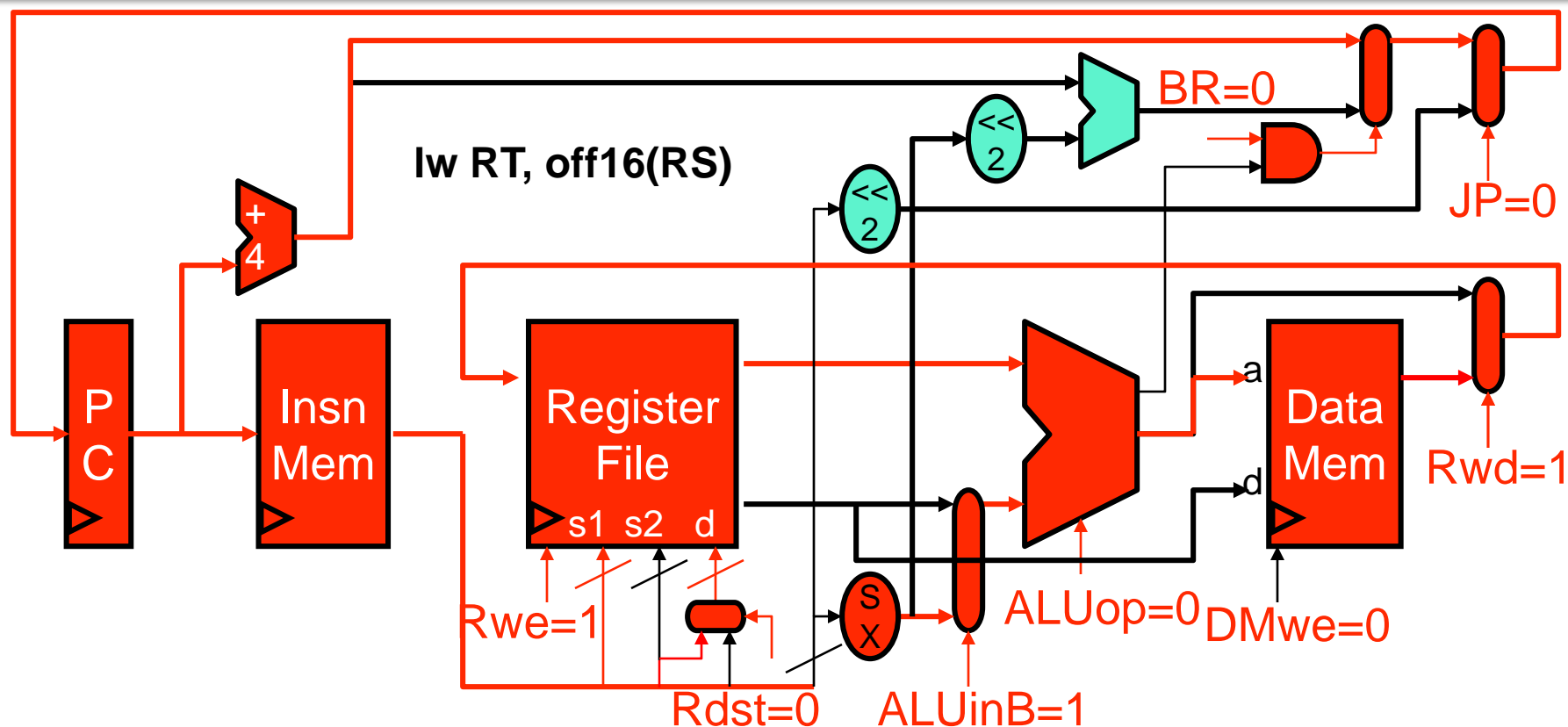

- Here is the solution

How Is Control Implemented?

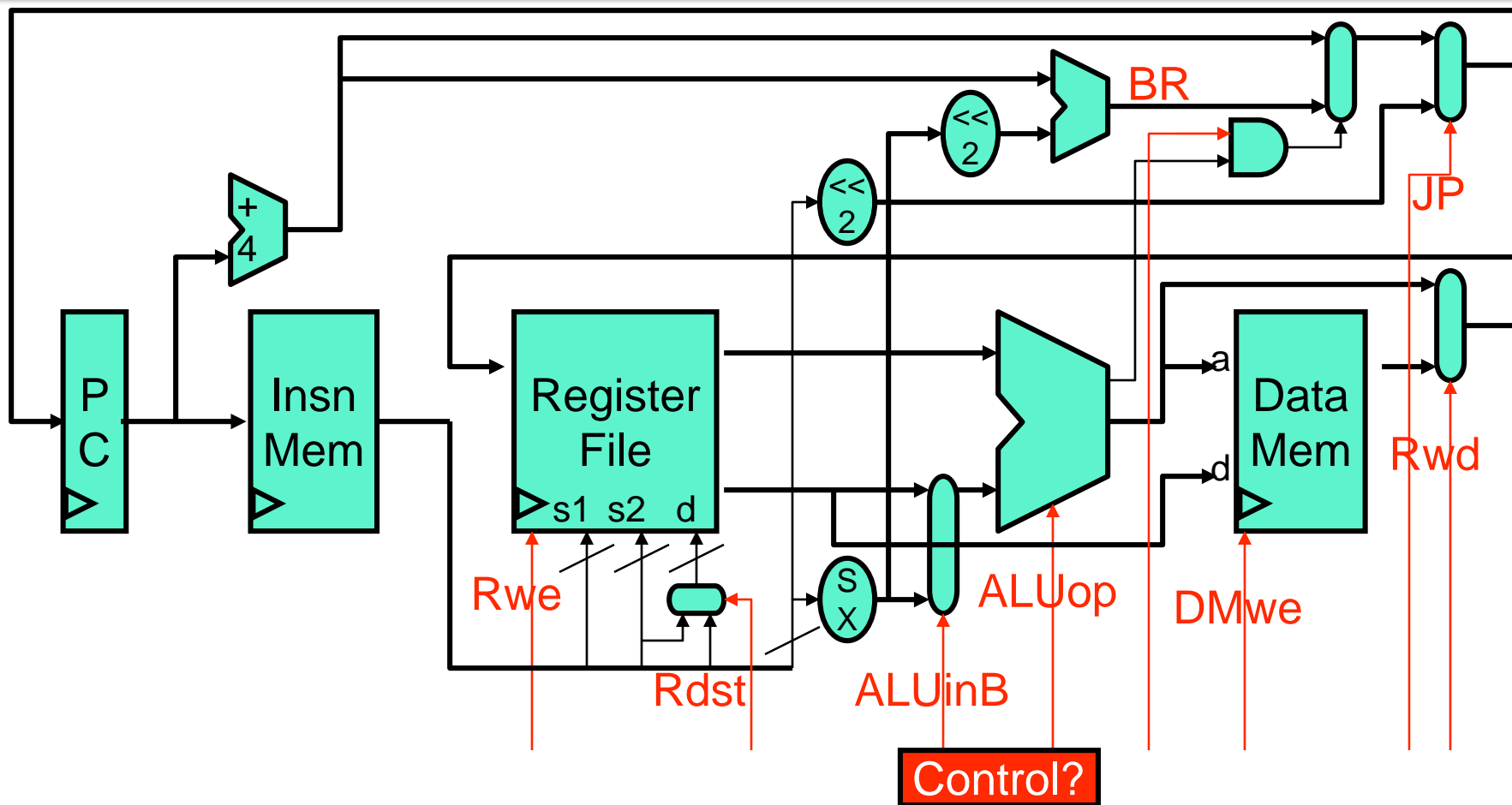


Implementing Control

- Each insn has a unique set of control signals
 - Most are function of opcode
 - Some may be encoded in the instruction itself
 - E.g., the ALUop signal is some portion of the MIPS Func field
 - + Simplifies controller implementation
 - Requires careful ISA design

Control Implementation: ROM

 
- **ROM (read only memory)**: think rows of bits
 - Bits in data words are control signals
 - Lines indexed by opcode
 - Example: ROM control for 6-insn MIPS datapath
 - X is “don’t care”




Control Implementation: Random Logic

- Real machines have 100+ insns 300+ control signals
 - 30,000+ control bits (~4KB)
 - Not huge, but hard to make faster than datapath (important!)
- Alternative: random logic (random = 'non-repeating')
 - Exploits the observation: many signals have few 1s or few 0s
 - Example: random logic control for 6-insn MIPS datapath

 Yes, "random logic" is a very dumb and misleading name for this concept. Sorry.



Datapath and Control Timing

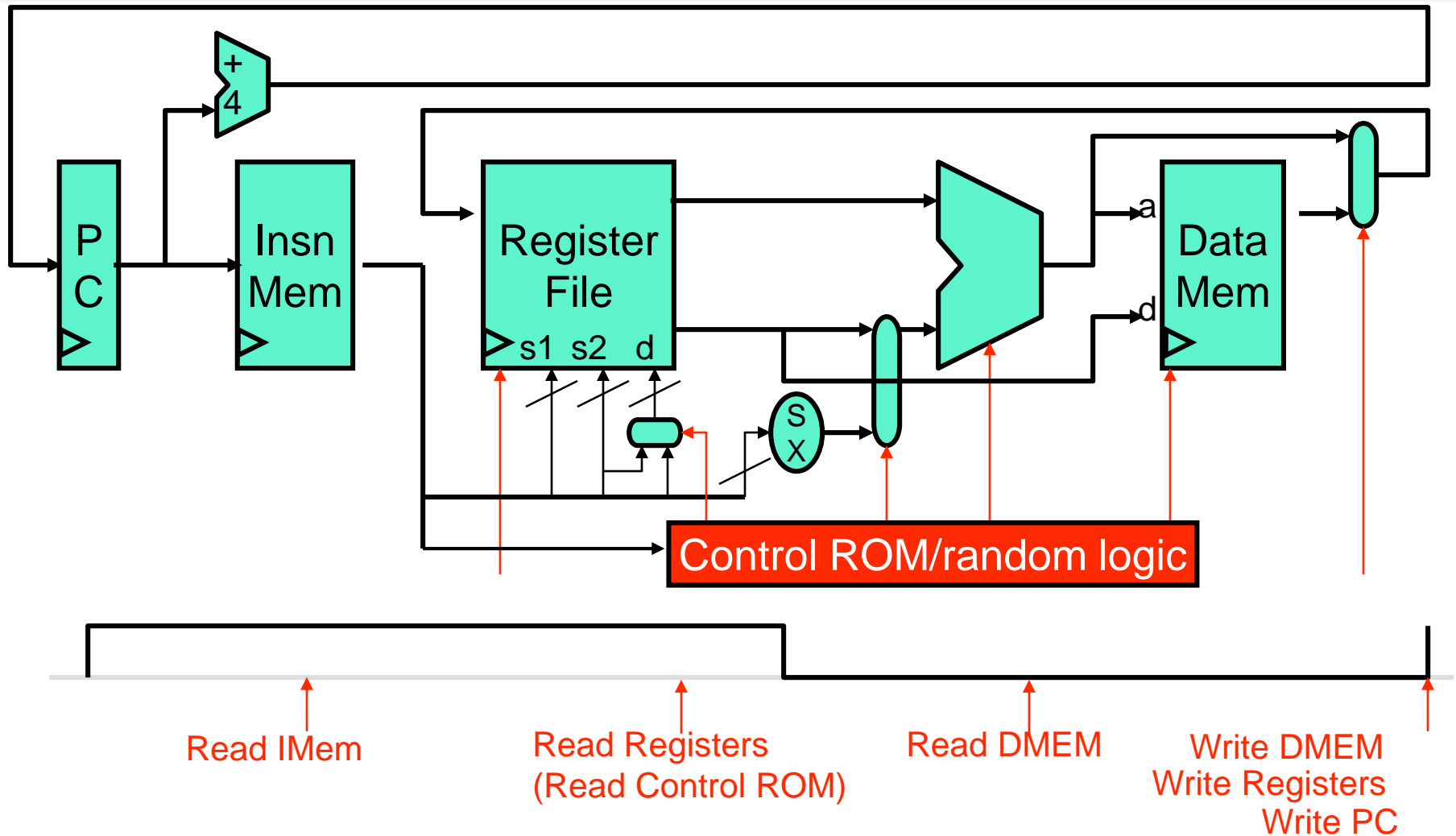

Summary

- Datapaths:
 - What do we need?
 - How do we control?
 - How are control signals implemented?